

# Chapter 7

## Two Port Network

# Terminologies


- Terminal

If a conductor is fastened to any nodes on the network and brought out for access, the end of this conductors is designated as a terminal.

- Port

A port is a pair of terminal such that the current entering into one terminal is exactly equal to the current leaving from another terminal.


# Single Port Network

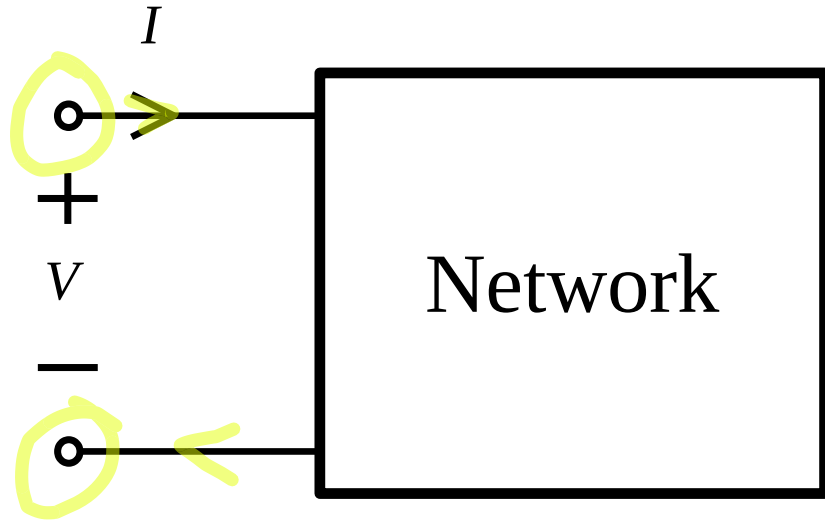

- Terminal Quantity ( $V$ ,  $I$ )
- Either connect current and measure voltage or connect voltage and measure current.

Note: Application is similar to Thevenin and Norton

# Two Port Network

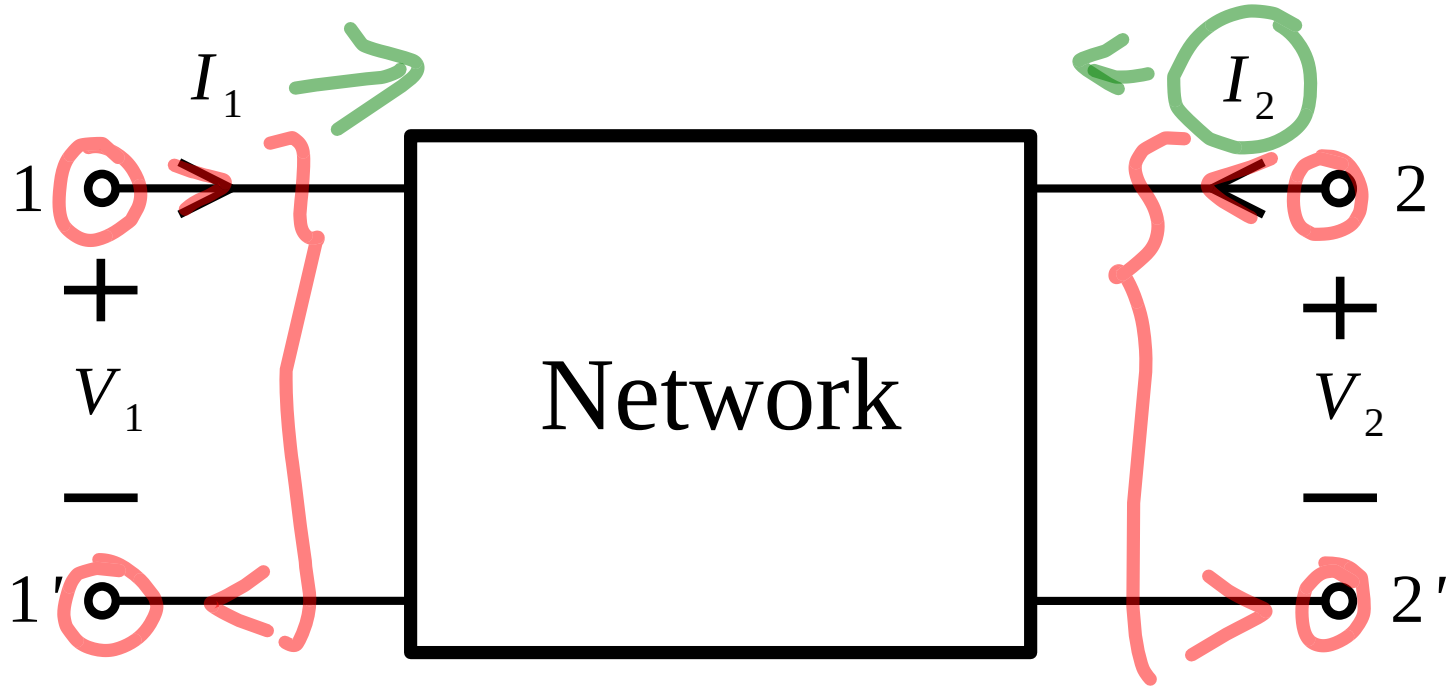

Note: The flow of current is into the network, which is a convention.

# Two Port Network

- Terminal Quantities

Port 1:  $V_1, I_1$  and Port 2:  $V_2, I_2$

- We want:

- a terminal description or,
- a port description or,
- an external description

of the system

# Two Port Network

- We can consider any two of the terminal quantities as an independent variable and other shall be dependent variables.
- Six possible description ( $4C_2$ ) 
$$\underline{V_1, I_1, V_2, I_2}$$
  - can set two as independent (by connecting sources) and find another two.

Note: We consider network that are linear and do not have any independent sources. But the network can have dependent sources.


S.N.	<u>Dependent</u> <u>Quantities</u> (Express)	<u>Independent</u> <u>Quantities</u> (In terms of)	Description
1	<u><math>V_1, V_2</math></u>	<u><math>I_1, I_2</math></u>	<u>Open-circuit impedance parameter</u> ( <u>z parameter</u> )
2	<u><math>I_1, I_2</math></u>	<u><math>V_1, V_2</math></u>	<u>Short-circuit admittance parameter</u> ( <u>y parameter</u> )
3	<u><math>V_1, I_1</math></u>	<u><math>V_2, I_2</math></u>	Transmission parameter <del>T-parameter</del> (ABCD parameter)

S.N.	Dependent Quantities (Express)	Independent Quantities (In terms of)	Description
4	<u><math>V_2, I_2</math></u>	<u><math>V_1, I_1</math></u>	<u>Inverse transmission parameter</u> <u>(A'B'C'D' parameter)</u>
5	<u><math>V_1, I_2</math></u>	<u><math>I_1, V_2</math></u>	<u>Hybrid parameter</u> <u>(h parameter)</u>
6	<u><math>I_1, V_2</math></u>	<u><math>V_1, I_2</math></u>	Inverse hybrid parameter (g parameter)



# Open-circuit Impedance Parameter (z parameter)

# z parameter

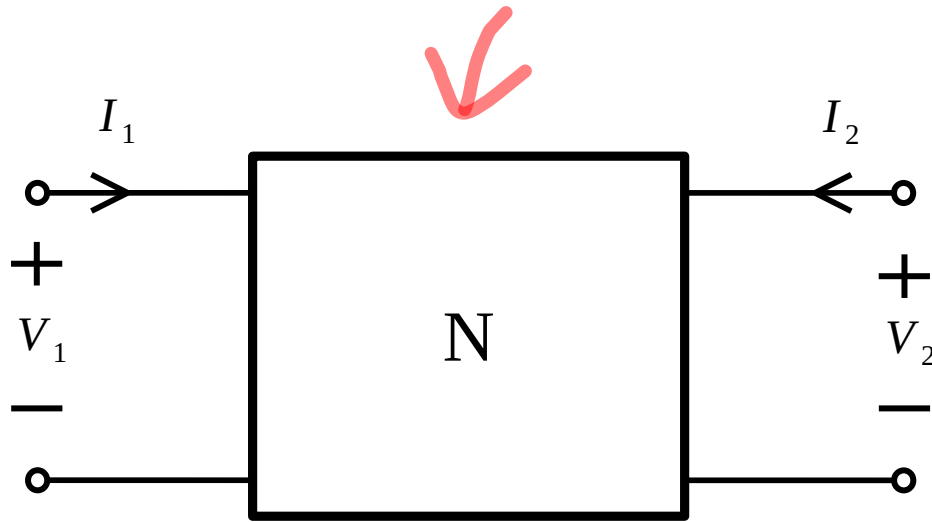

- Express  $V_1$ ,  $V_2$  in terms of  $I_1$  and  $I_2$


$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\underline{Z_{11}}$$

- From definition:

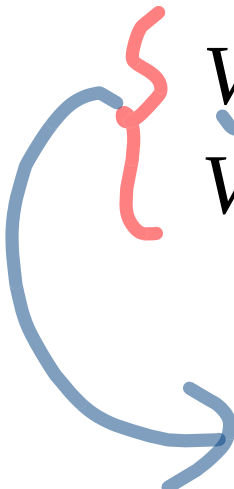
$$\begin{cases} V_1 = z_{11} I_1 + z_{12} I_2 \\ V_2 = z_{21} I_1 + z_{22} I_2 \end{cases}$$

$$z_{11} = \frac{V_1}{I_1} \bigg|_{I_2 = 0}$$


- Driving point impedance at port 1 with port 2 open.
- Also called open circuit driving point input impedance.



$$Z_{11}$$

- Driving point  
impedance at port 1  
with port 2 open.

$$Z_{11} = \frac{V_1}{I_1} \bigg|_{I_2 = 0}$$

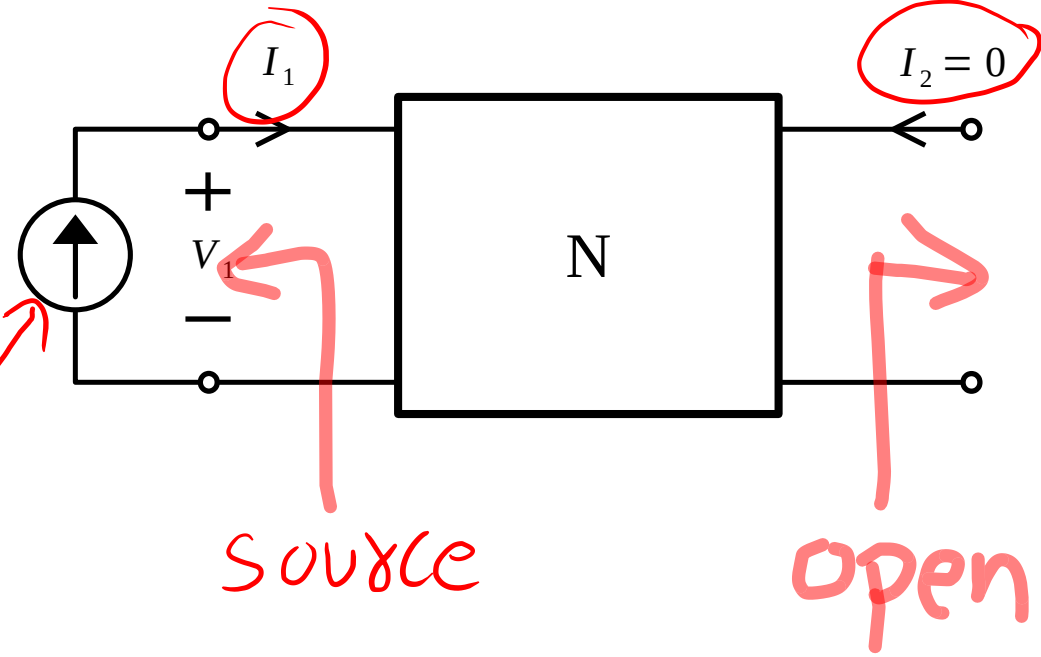

$$\underline{Z_{12}}$$

- From definition:

$$\begin{aligned} V_1 &= z_{11} I_1 + z_{12} I_2 \\ V_2 &= z_{21} I_1 + z_{22} I_2 \end{aligned}$$


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1 = 0}$$

- Transfer impedance from port 2 to port 1 with port 1 open.
- Also called open circuit reverse transfer impedance.

$$Z_{12}$$

- Transfer impedance from port 2 to port 1 with port 1 open.

$$Z_{12} = \frac{V_1}{I_2} \quad | \quad I_1 = 0$$

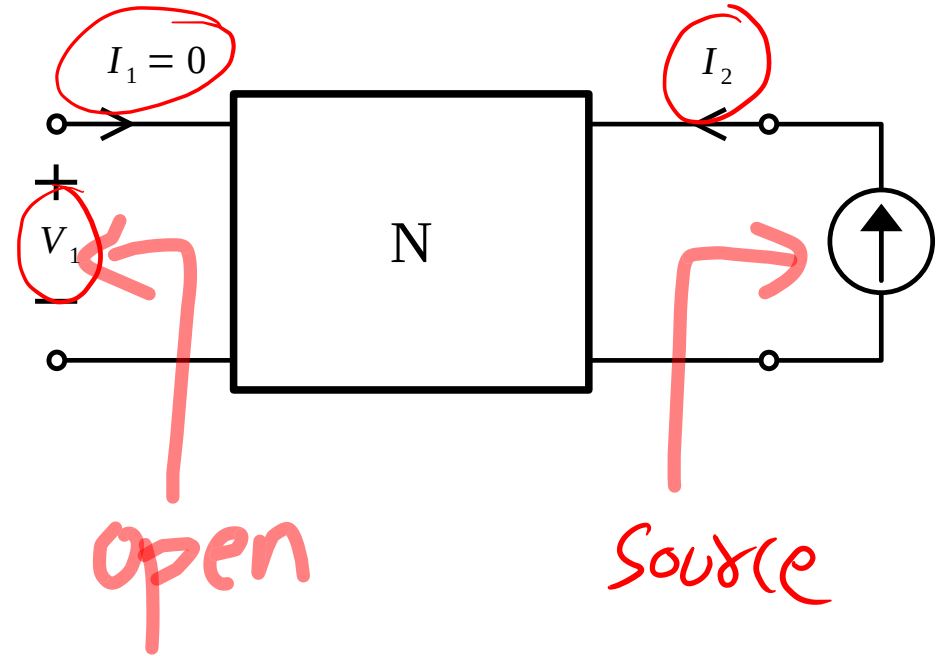

## Z<sub>21</sub>

- From definition:

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$


$$z_{21} = \frac{V_2}{I_1} \bigg|_{I_2=0}$$

- Transfer impedance from port 1 to port 2 with port 2 open.
- Also called open circuit forward transfer impedance.

$Z_{21}$

- Transfer impedance from port 1 to port 2 with port 2 open.

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2 = 0}$$

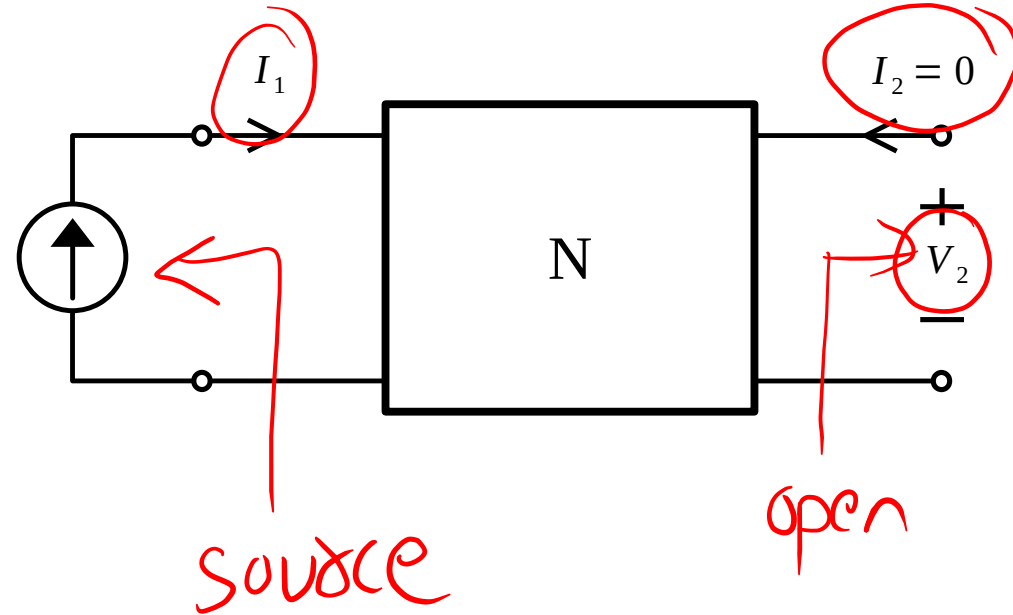



$$Z_{22}$$

- From definition:

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$


$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1 = 0}$$

- Driving point impedance at port 2 with port 1 open.
- Also called open circuit driving point output impedance.

$Z_{22}$

- Driving point impedance at port 2 with port 1 open.

$$Z_{22} = \frac{V_2}{I_2} \bigg|_{I_1 = 0}$$

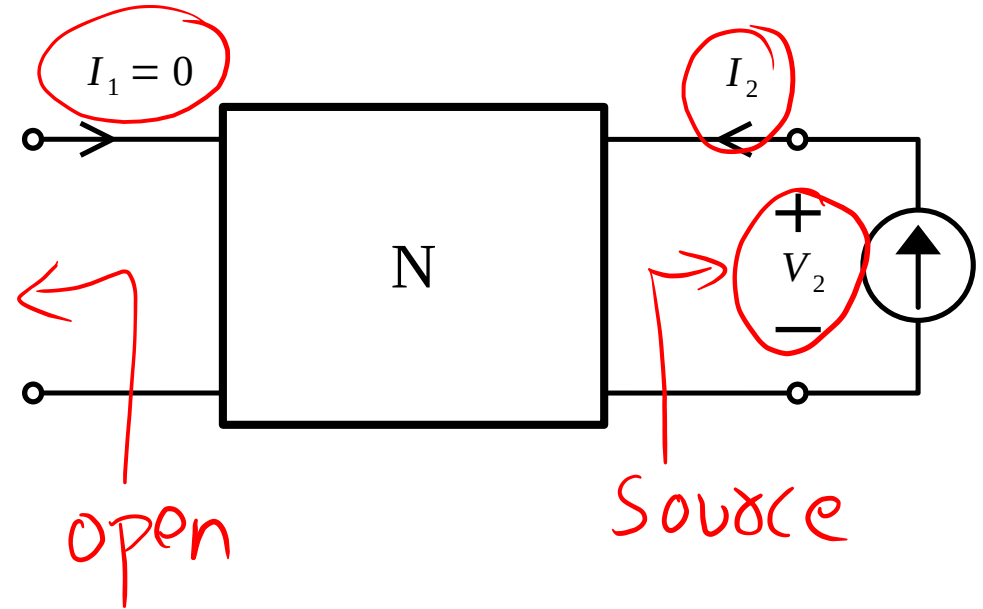

# Open-circuit Impedance Parameter

- z parameter are also called open-circuit impedance parameter because, each parameter is determined by open circuiting either port 1 or port 2.

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2 = 0}$$


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1 = 0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2 = 0}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1 = 0}$$

# Short-circuit Admittance Parameter (y parameter)

# y parameter

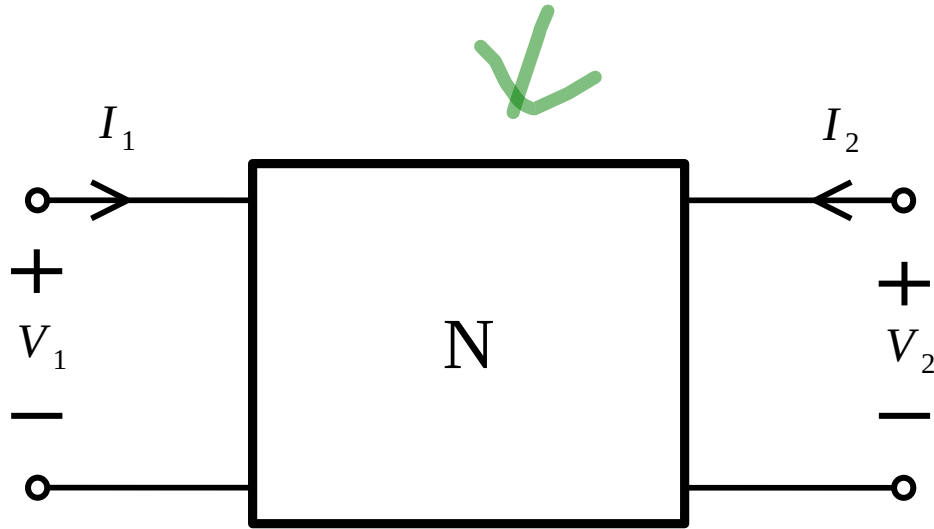

- Express  $I_1$ ,  $I_2$  in terms of  $V_1$  and  $V_2$

$$\begin{aligned} \check{I}_1 &= \check{y}_{11} \check{V}_1 + \check{y}_{12} \check{V}_2 \\ \check{I}_2 &= \check{y}_{21} \check{V}_1 + \check{y}_{22} \check{V}_2 \end{aligned}$$
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\underline{y_{11}}$$

- From definition:

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$


$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2 = 0}$$

- Driving point admittance at port 1 with port 2 short circuited.
- Also called short circuit driving point input admittance.

$$y_{11}$$

- Driving point admittance at port 1 with port 2 short circuited.

$$y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0}$$

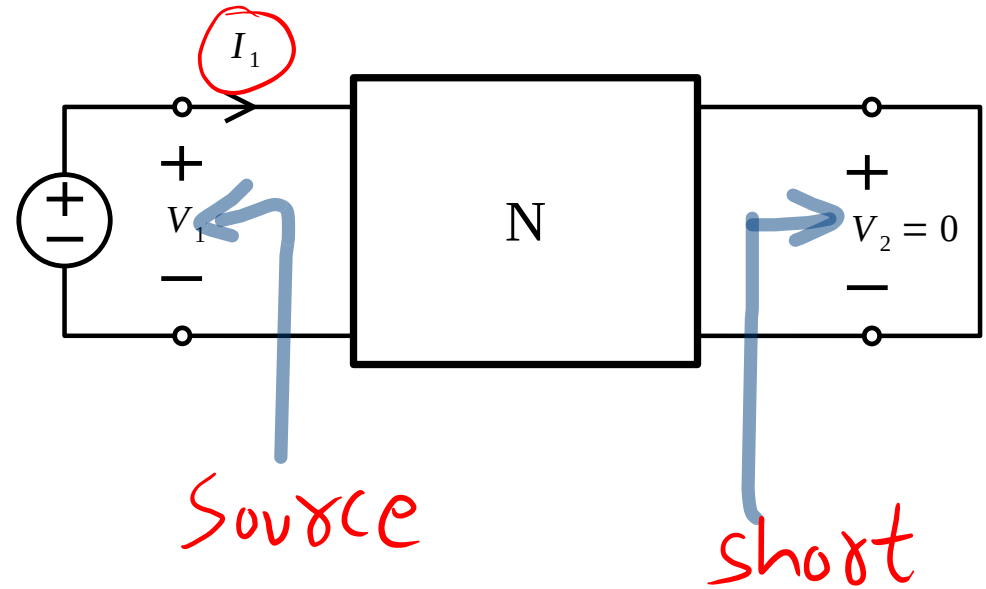

$$\underline{y_{12}}$$

- From definition:

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$

$$y_{12} = \frac{I_1}{V_2} \bigg|_{V_1 = 0}$$


- Transfer admittance from port 2 to port 1 with port 1 short circuited.
- Also called short circuit reverse transfer admittance.



$$y_{12}$$

- Transfer admittance from port 2 to port 1 with port 1 short circuited.

$$y_{12} = \frac{I_1}{V_2} \bigg|_{V_1 = 0}$$

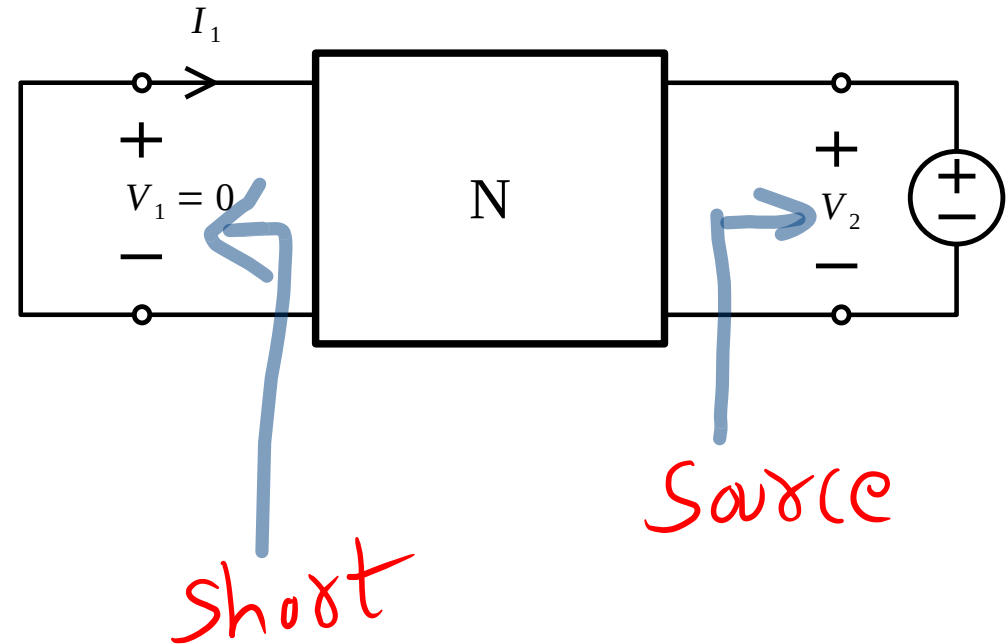

$$y_{21}$$

- From definition:

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$


$$y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$

- Transfer admittance from port 1 to port 2 with port 2 short circuited.
- Also called short circuit forward transfer admittance.

$$y_{21}$$

- Transfer admittance from port 1 to port 2 with port 2 short circuited.

$$\underline{y_{21}} = \frac{\underline{I_2}}{\underline{V_1}} \bigg|_{V_2 = 0}$$

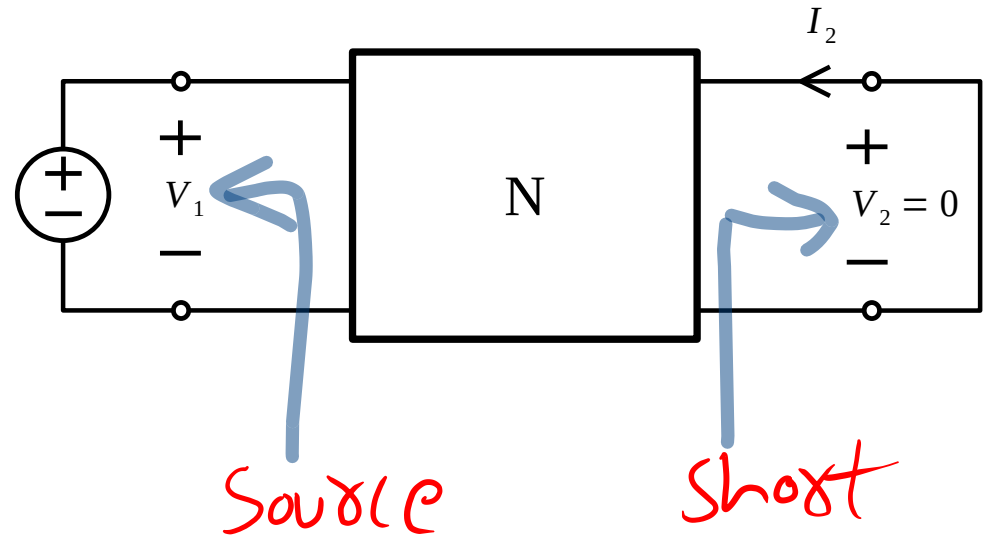

$$\underline{y_{22}}.$$

- From definition:

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$\underline{I_2} = y_{21} \underline{V_1} + \underline{y_{22}} \underline{V_2}$$


$$y_{22} = \left. \frac{\underline{I_2}}{\underline{V_2}} \right|_{\underline{V_1 = 0}}$$

- Driving point admittance at port 2 with port 1 short circuited.
- Also called short circuit driving point output admittance.

$$y_{22}$$

- Driving point admittance at port 2 with port 1 short circuited.

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1 = 0}$$

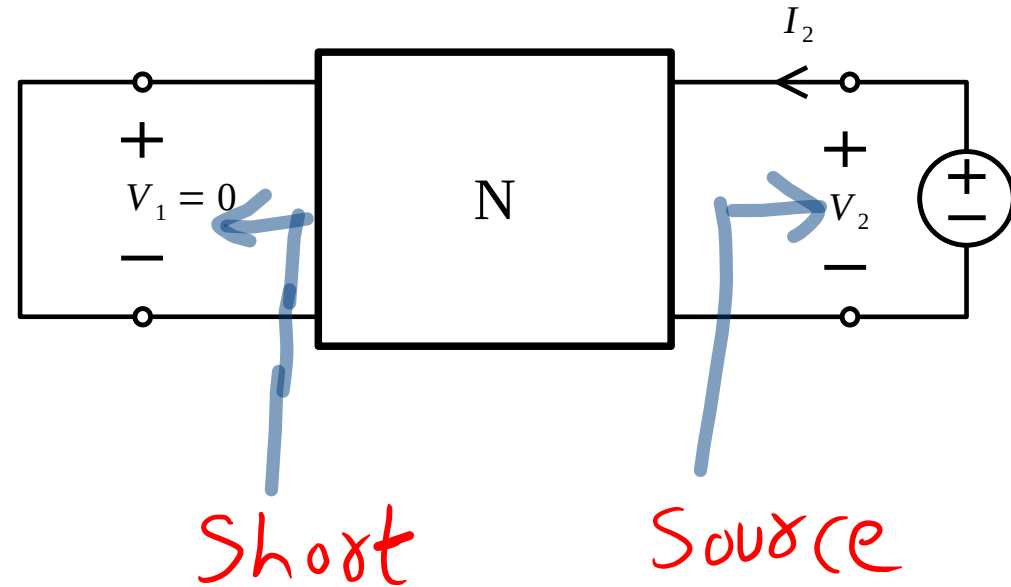

# Short-circuit Admittance Parameter

- y parameter are also called short-circuit admittance parameter because, each parameter is determined by short circuiting either port 1 or port 2.

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2 = 0}^{sc}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1 = 0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2 = 0}^{sc}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1 = 0}$$

Communication  
cascade


$$\begin{cases} V_1 = AV_2 + B(-I_2) \\ I_1 = C V_2 + D(-I_2) \end{cases}$$

Transmission Parameter  
(ABCD parameter)


$$\begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

T-parameter

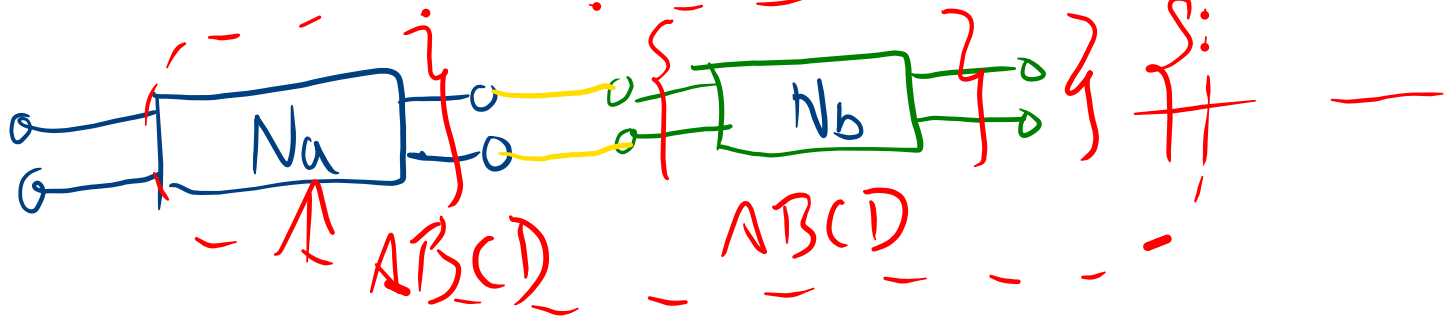inverse  $\uparrow$   $\begin{pmatrix} T \\ T' \end{pmatrix}$



# Transmission Parameter

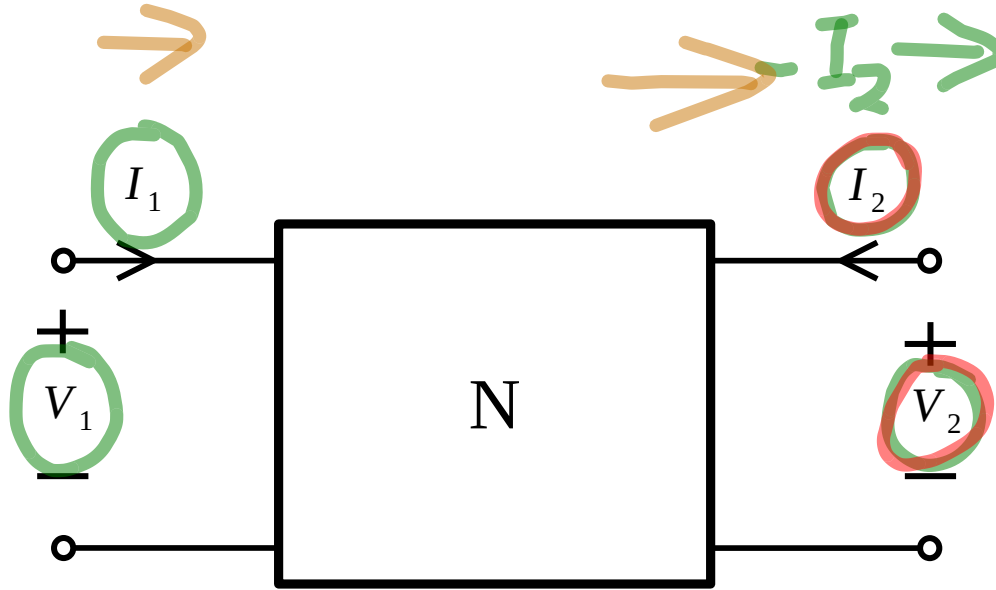

- Express  $V_1, I_1$  in terms of  $V_2$  and  $-I_2$

$$\begin{aligned} V_1 &= A V_2 - B I_2 \\ I_1 &= C V_2 - D I_2 \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$



A

- From definition:

$$\begin{cases} V_1 = A V_2 - B I_2 \\ I_1 = C V_2 - D I_2 \end{cases}$$

- Reciprocal of open  
circuit forward voltage  
transfer function


$V_1$   $(V_2, I_2)$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{\left. \frac{V_2}{V_1} \right|_{I_2=0}}$$

Diagram illustrating the definition of the parameter A. The left side shows the ratio  $V_1/V_2$  with  $I_2=0$  (open circuit at port 2). The right side shows the reciprocal ratio  $V_2/V_1$  with  $I_2=0$  (open circuit at port 2). Red arrows and circled numbers 1 and 2 indicate the relationship between the two ratios.

A

$$A = \frac{1}{\left. \frac{V_2}{V_1} \right|_{I_2 = 0}}$$

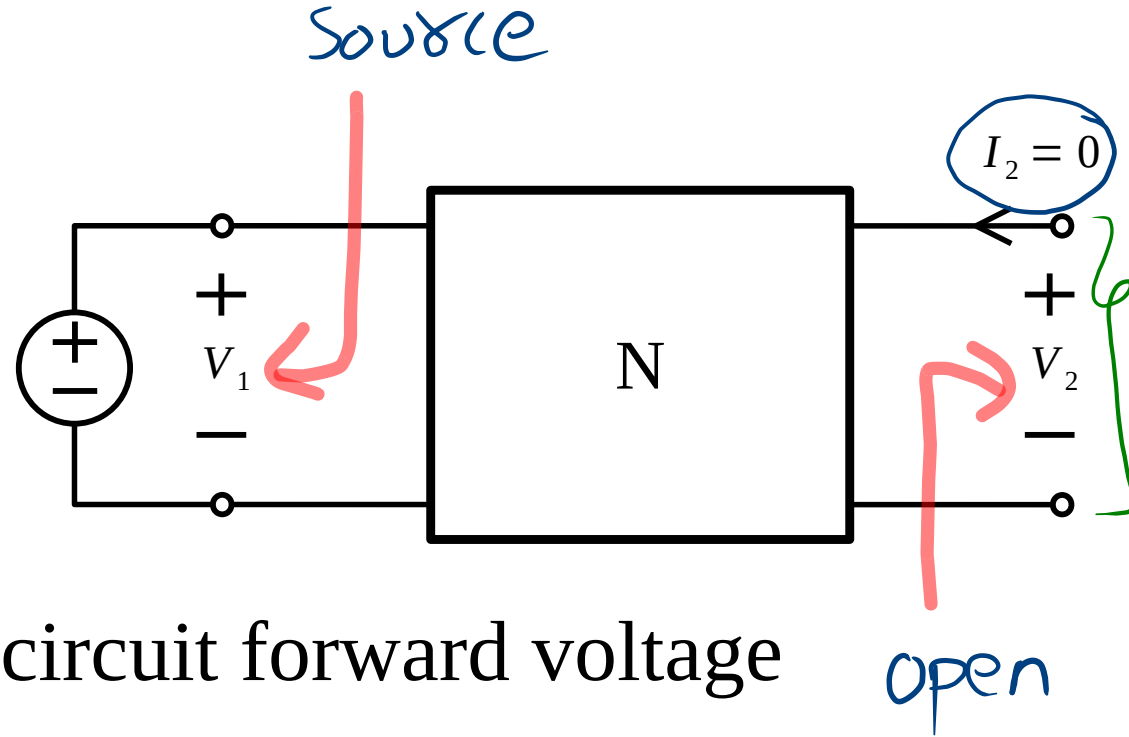

- Reciprocal of open circuit forward voltage transfer function

# B



- From definition:

$$\begin{aligned} V_1 &= A V_2 - B I_2 \\ I_1 &= C V_2 - D I_2 \end{aligned}$$

- Reciprocal of short circuit forward transfer admittance function

$$B = \frac{V_1}{-I_2} \bigg|_{V_2 = 0} = \frac{1}{-I_2}$$

# B

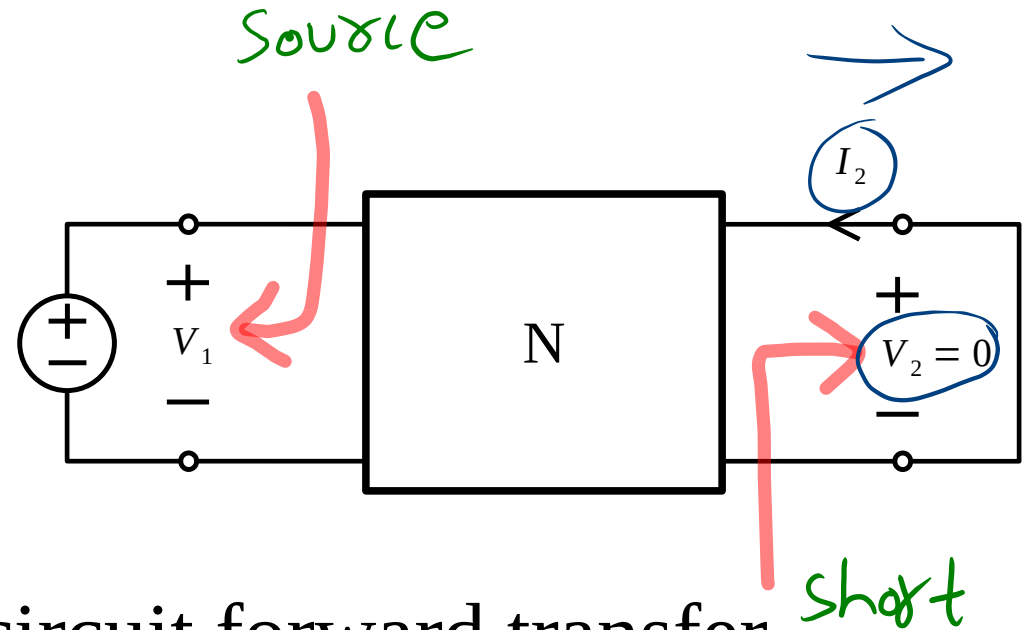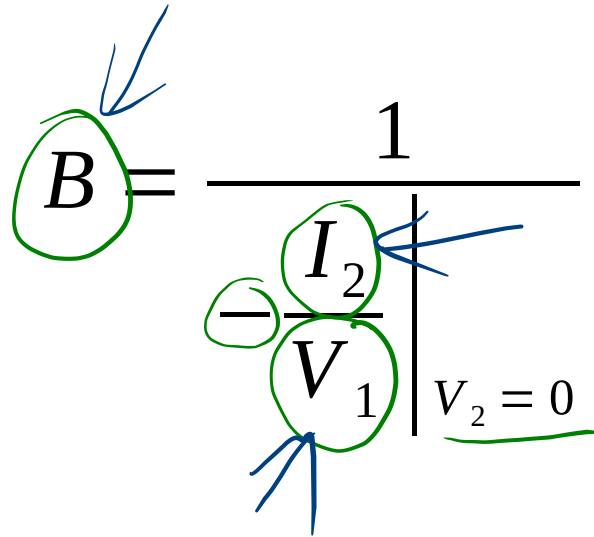

- Reciprocal of short circuit forward transfer admittance function


C

- From definition:


$$V_1 = A V_2 - B I_2$$

$$I_1 = \underline{C} V_2 - D \textcircled{I_2}$$

- Reciprocal of open circuit forward transfer impedance function

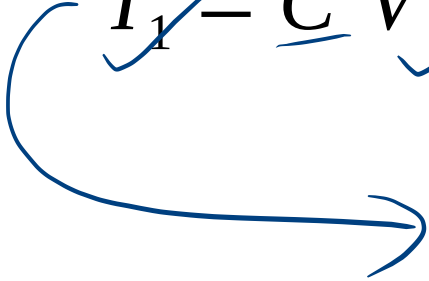
$$C = \frac{\cancel{I_1}}{\cancel{V_2} \textcircled{I_2 = 0}} = \frac{1}{\frac{\textcircled{V_2}}{\textcircled{I_1}} \textcircled{I_2 = 0}}$$

C

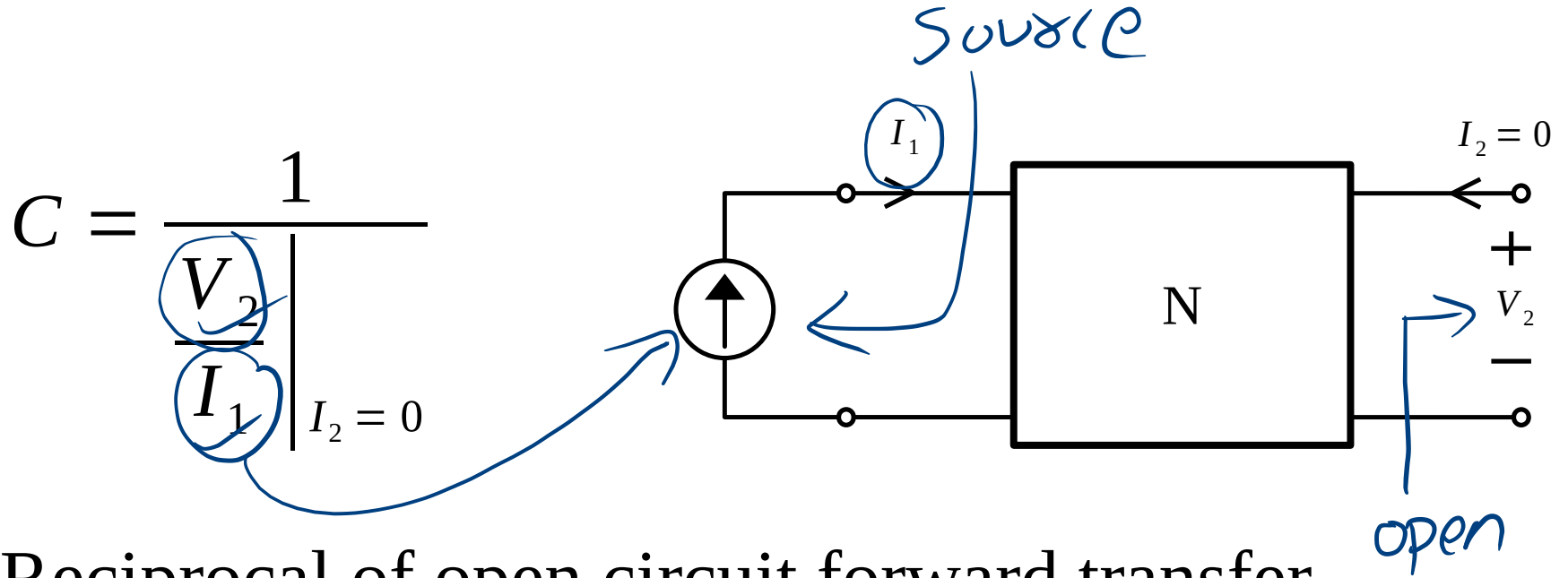

- Reciprocal of open circuit forward transfer impedance function

D

- From definition:


$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - \underline{D} I_2$$

- Reciprocal of short circuit forward current transfer function

$$D = \frac{I_1}{-I_2} \bigg|_{V_2=0} = \frac{1}{-\frac{I_2}{I_1} \bigg|_{V_2=0}}$$

# D

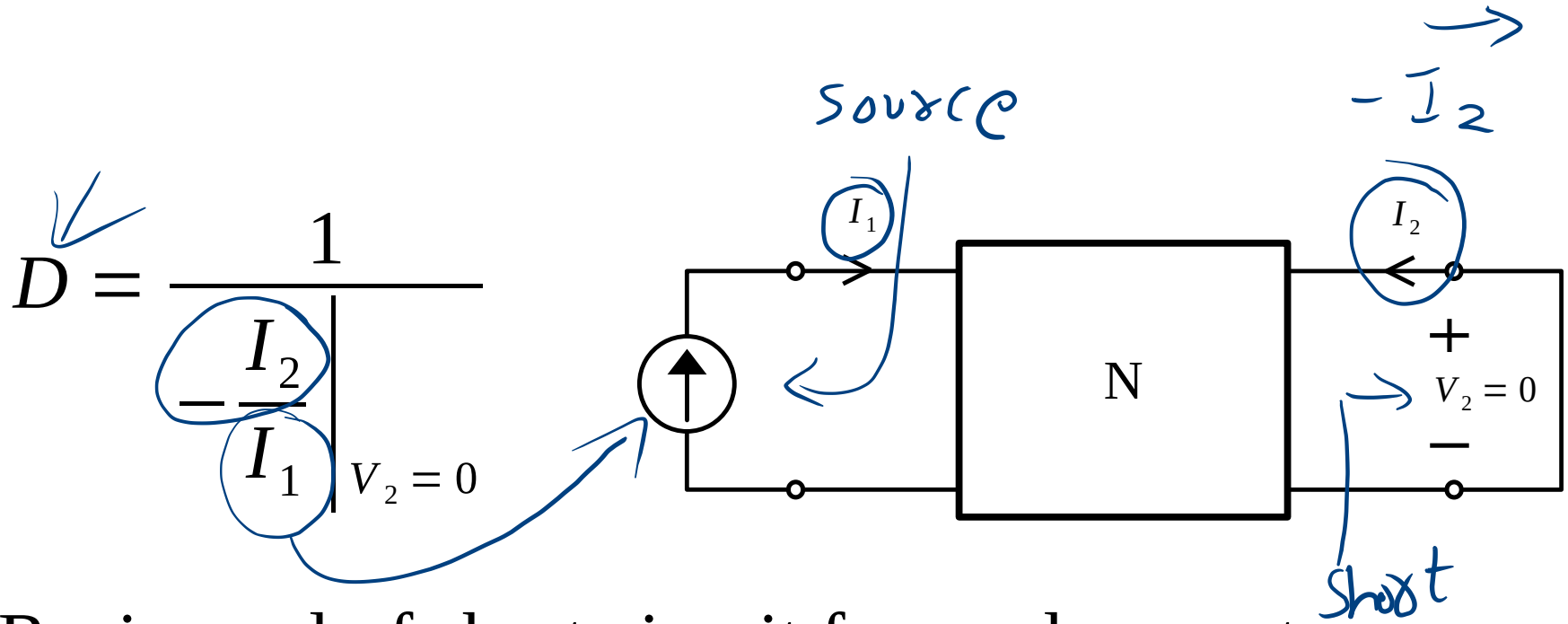

- Reciprocal of short circuit forward current transfer function



# Transmission Parameter

- From definition:

$$\begin{cases} V_1 = A V_2 - B I_2 \\ I_1 = C V_2 - D I_2 \end{cases}$$

$$\underline{A} = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \text{transfer}$$

$$\underline{C} = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \text{transfer}$$

$$\underline{B} = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \text{transfer}$$

$$\underline{D} = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \quad \text{transfer}$$

# Transmission Parameter


<u>A</u>	Reciprocal of open circuit forward voltage <u>transfer function</u>
<u>B</u>	Reciprocal of short circuit forward <u>transfer admittance function</u>
<u>C</u>	Reciprocal of open circuit forward <u>transfer impedance function</u>
<u>D</u>	Reciprocal of short circuit forward current <u>transfer function</u>

Note: ABCD parameter are all transfer functions relating quantity of one port to another port.

# Inverse Transmission Parameter (A' B' C' D' parameter)

$T'$

# Inverse Transmission Parameter

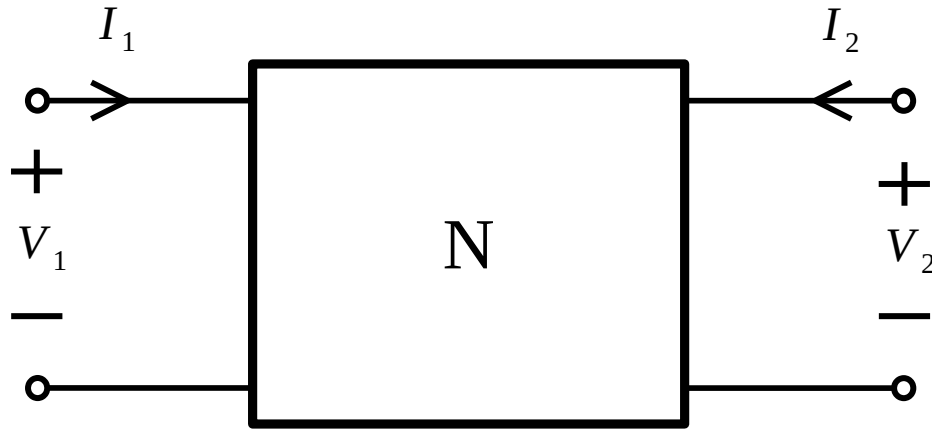

- Express  $V_2$ ,  $I_2$  in terms of  $V_1$  and  $-I_1$

$$V_2 = A' V_1 - B' I_1$$

$$I_2 = C' V_1 - D' I_1$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

# Inverse Transmission Parameter

- From definition:

$$\begin{cases} \underline{V}_2 = \underline{A}' \underline{V}_1 - \underline{B}' \underline{I}_1 \\ \underline{I}_2 = \underline{C}' \underline{V}_1 - \underline{D}' \underline{I}_1 \end{cases}$$

$$\underline{A}' = \left. \frac{\underline{V}_2}{\underline{V}_1} \right|_{\underline{I}_1 = 0} \quad \text{transfer}$$

$$\underline{C}' = \left. \frac{\underline{I}_2}{\underline{V}_1} \right|_{\underline{I}_1 = 0} \quad \text{transfer}$$


$$\underline{B}' = \left. \frac{\underline{V}_2}{-\underline{I}_1} \right|_{\underline{V}_1 = 0} \quad \text{transfer}$$

$$\underline{D}' = \left. \frac{\underline{I}_2}{-\underline{I}_1} \right|_{\underline{V}_1 = 0} \quad \text{transfer}$$


Electronics  
Circuit

transistor

## Hybrid Parameter (h parameter)

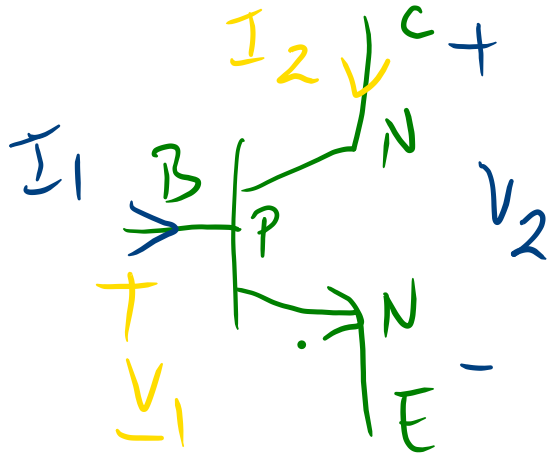

# h parameter

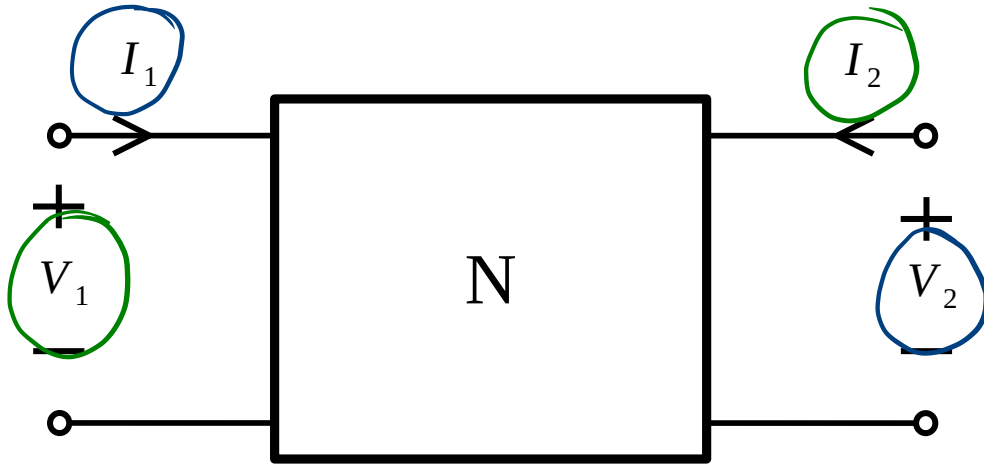

- Express  $V_1$ ,  $I_2$  in terms of  $I_1$  and  $V_2$

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

The equations and matrix are annotated with green and blue circles and brackets, corresponding to the variable circles in the diagram. A green arrow points from the equations to the matrix representation.

$$\underline{h_{11}}$$

- From definition:

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$


- Driving point impedance at port 1 with port 2 short circuited.
- Also called short circuit driving point input impedance.



$h_{11}$ 

- Driving point impedance at port 1 with port 2 short circuited.

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2 = 0}$$

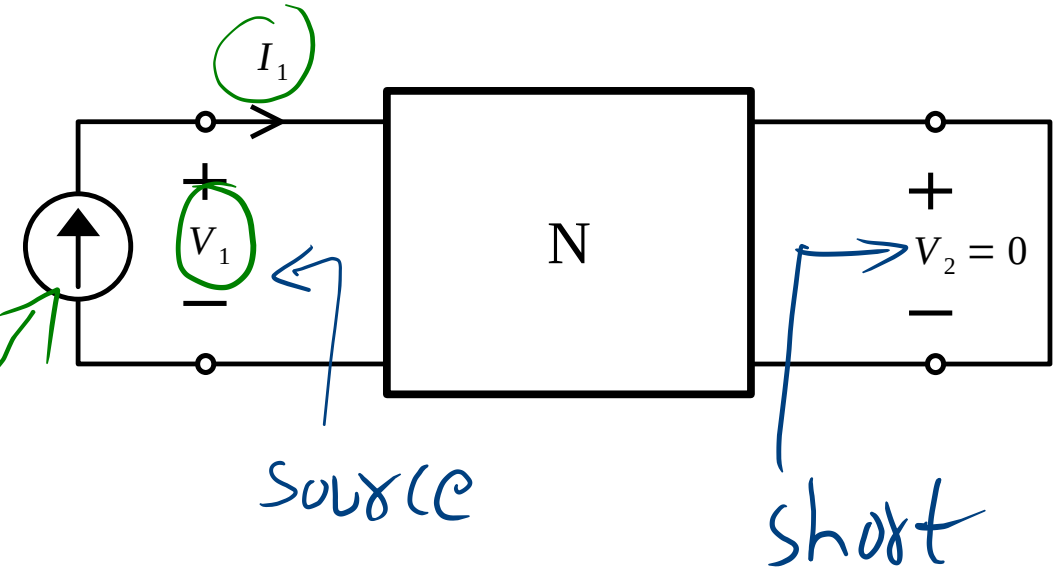

## $h_{12}$

- From definition:

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$


$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1 = 0}$$

- Voltage transfer from port 2 to port 1 with port 1 open circuited.
- Also called open circuit reverse voltage transfer function.

$h_{12}$ 

- Voltage transfer from port 2 to port 1 with port 1 open circuited.

$$\underline{h_{12}} = \frac{V_1}{V_2} \bigg|_{\substack{I_1 = 0 \\ \text{open}}}$$

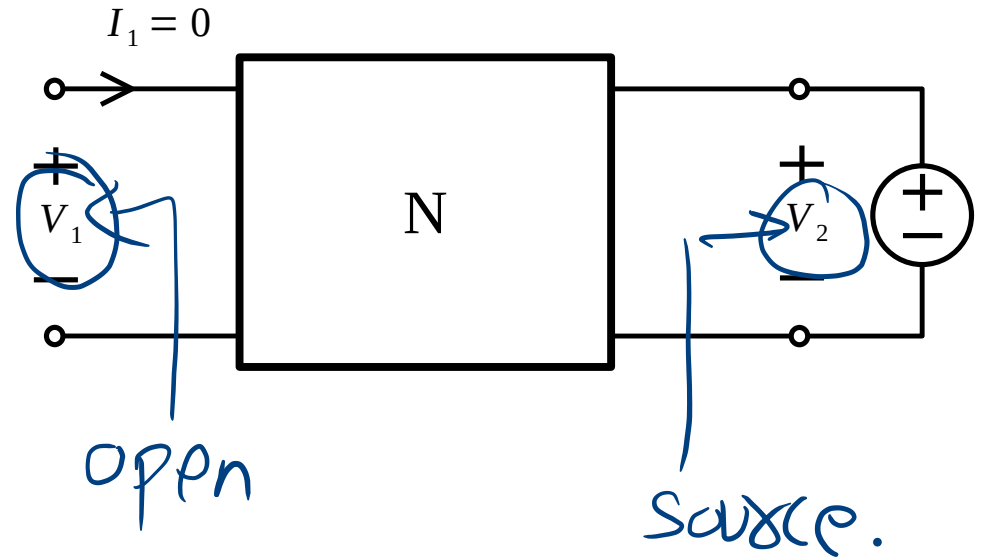

$h_{21}$

- From definition:

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$


$h_{21} = \frac{I_2}{I_1} \bigg|_{V_2 = 0}$

- Current transfer from port 1 to port 2 with port 2 short circuited.
- Also called short circuit forward current transfer function.

$h_{21}$

- Current transfer from port 1 to port 2 with port 2 short circuited.

$$\underline{h_{21}} = \frac{\underline{I_2}}{\underline{I_1}} \bigg|_{\textcircled{V_2 = 0}}$$

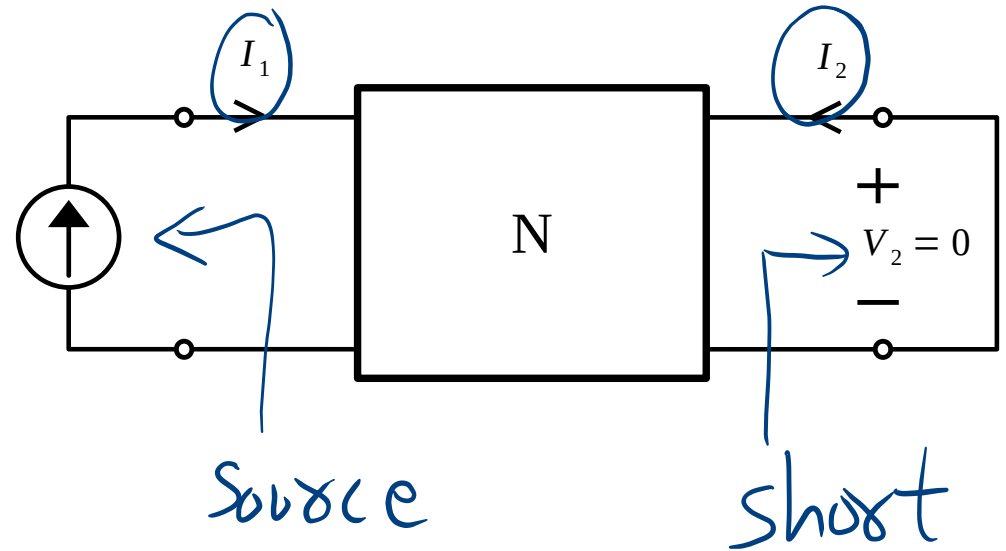

$$\underline{h_{22}}$$

- From definition:

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ \underline{I_2} &= h_{21} \underline{I_1} + \underline{h_{22}} \underline{V_2} \end{aligned}$$


$$\underline{h_{22}} = \frac{\underline{I_2}}{\underline{V_2}} \bigg|_{\underline{I_1} = 0}$$

- Driving point admittance at port 2 with port 1 open circuited.
- Also called open circuit driving point output admittance.

$h_{22}$

- Driving point admittance at port 2 with port 1 open circuited.

$$\underline{h_{22}} = \frac{\underline{I_2}}{\underline{V_2}} \bigg|_{\textcircled{I_1 = 0}}$$

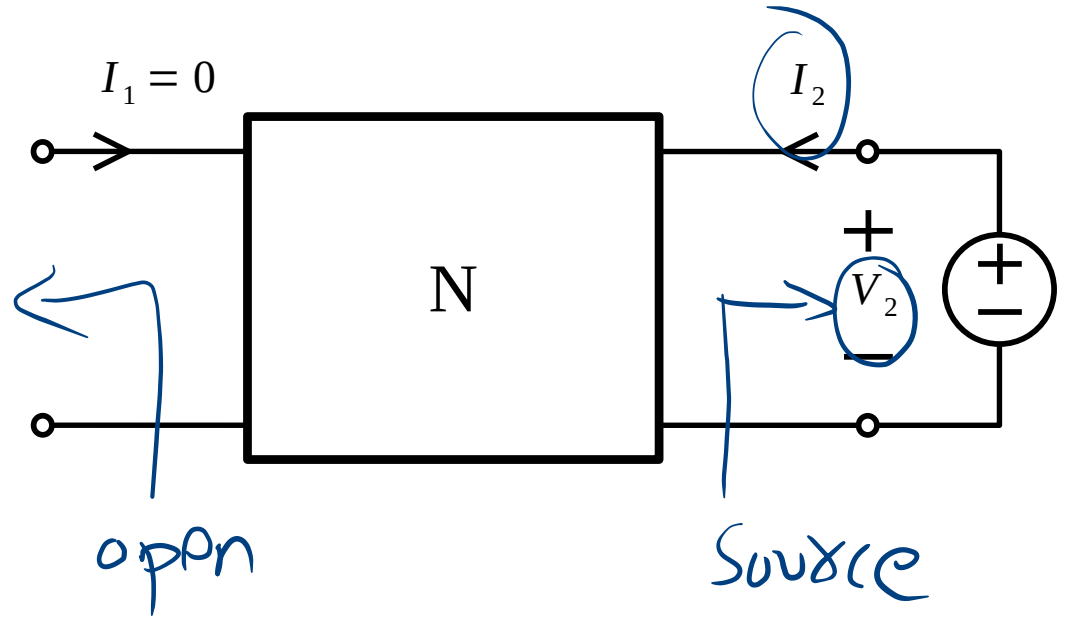

# h Parameter

- From definition:

$$\underline{V}_1 = h_{11} \underline{I}_1 + h_{12} \underline{V}_2$$
$$\underline{I}_2 = h_{21} \underline{I}_1 + h_{22} \underline{V}_2$$

$$\underline{h}_{11} = \left. \frac{V_1}{I_1} \right|_{\substack{\text{impedance} \\ \text{d.p.} \\ V_2 = 0 \text{ s.c.}}}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{\substack{\text{ratio} \\ V_2 = 0 \text{ s.c.}}}$$


$$h_{12} = \left. \frac{V_1}{V_2} \right|_{\substack{\text{ratio} \\ I_1 = 0 \text{ o.c.}}}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{\substack{\text{admittance} \\ \text{d.p.} \\ I_1 = 0 \text{ o.c.}}}$$



# Inverse Hybrid Parameter (g parameter)

# g parameter

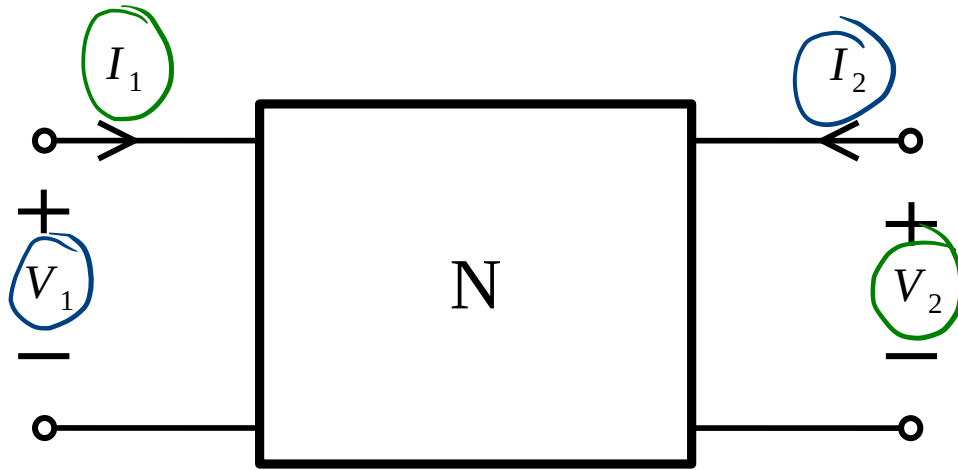

- Express  $I_1$ ,  $V_2$  in terms of  $V_1$  and  $I_2$

$$\begin{aligned} I_1 &= g_{11} V_1 + g_{12} I_2 \\ V_2 &= g_{21} V_1 + g_{22} I_2 \end{aligned}$$
$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

# g Parameter

- From definition:

$$\underline{I_1} = g_{11} \underline{V_1} + g_{12} \underline{I_2}$$
$$\underline{V_2} = g_{21} \underline{V_1} + g_{22} \underline{I_2}$$

$$\underline{g_{11}} = \left. \frac{\underline{I_1}}{\underline{V_1}} \right|_{\substack{\text{admittance} \\ \text{O.C.}}} \quad (I_2 = 0)$$

$$\underline{g_{21}} = \left. \frac{\underline{V_2}}{\underline{V_1}} \right|_{\substack{\text{ratio} \\ \text{O.C.}}} \quad (I_2 = 0)$$

$$\underline{g_{12}} = \left. \frac{\underline{I_1}}{\underline{I_2}} \right|_{\substack{\text{ratio} \\ \text{S.C.}}} \quad (V_1 = 0)$$

$$\underline{g_{22}} = \left. \frac{\underline{V_2}}{\underline{I_2}} \right|_{\substack{\text{impedance} \\ \text{S.C.}}} \quad (V_1 = 0)$$