

# RC circuit


$t = 0$

$R = 1\text{ k}\Omega$


$$v(t) = 5e^{-50t}$$

$$v_c(t) \quad C = 20\text{ }\mu\text{F}$$


Find  $i(t)$  and  $v_c(t)$

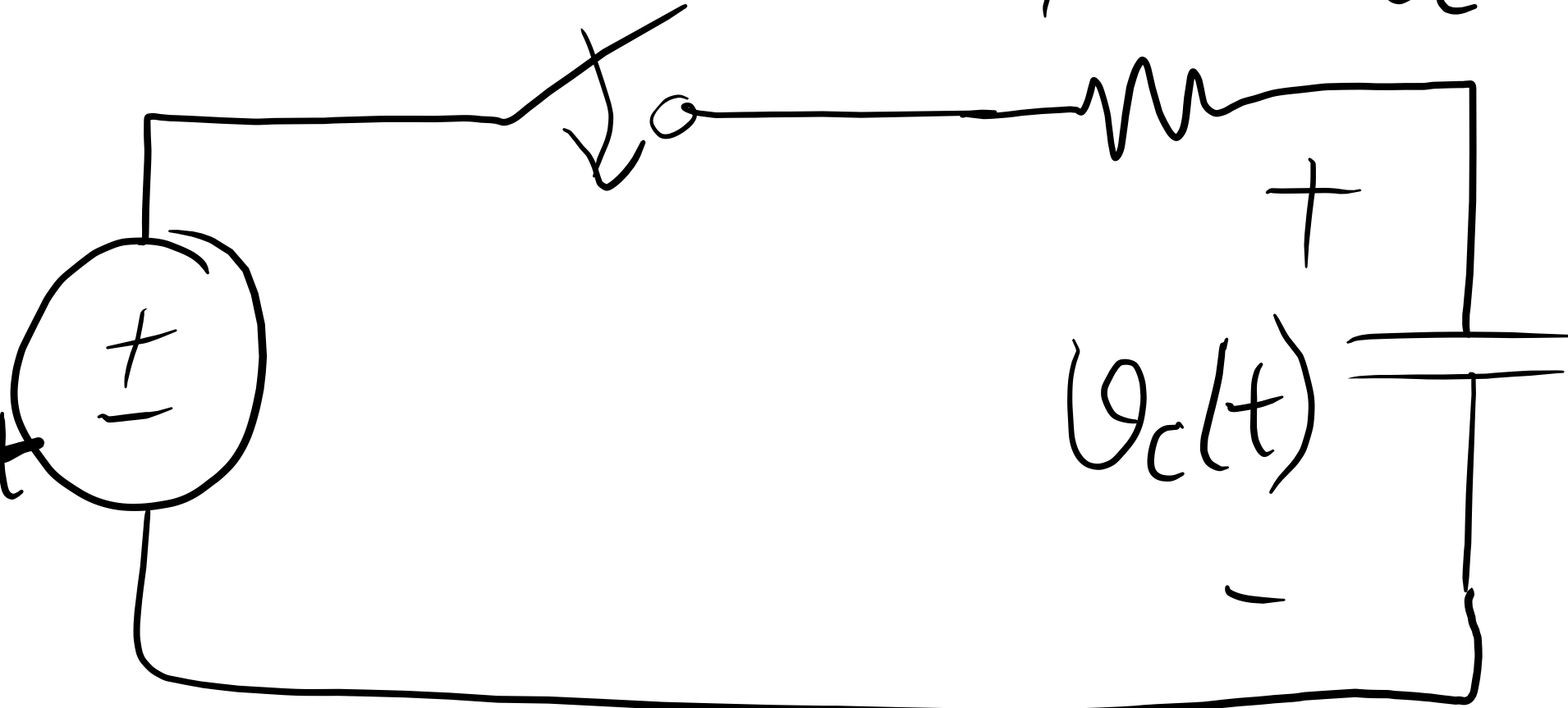

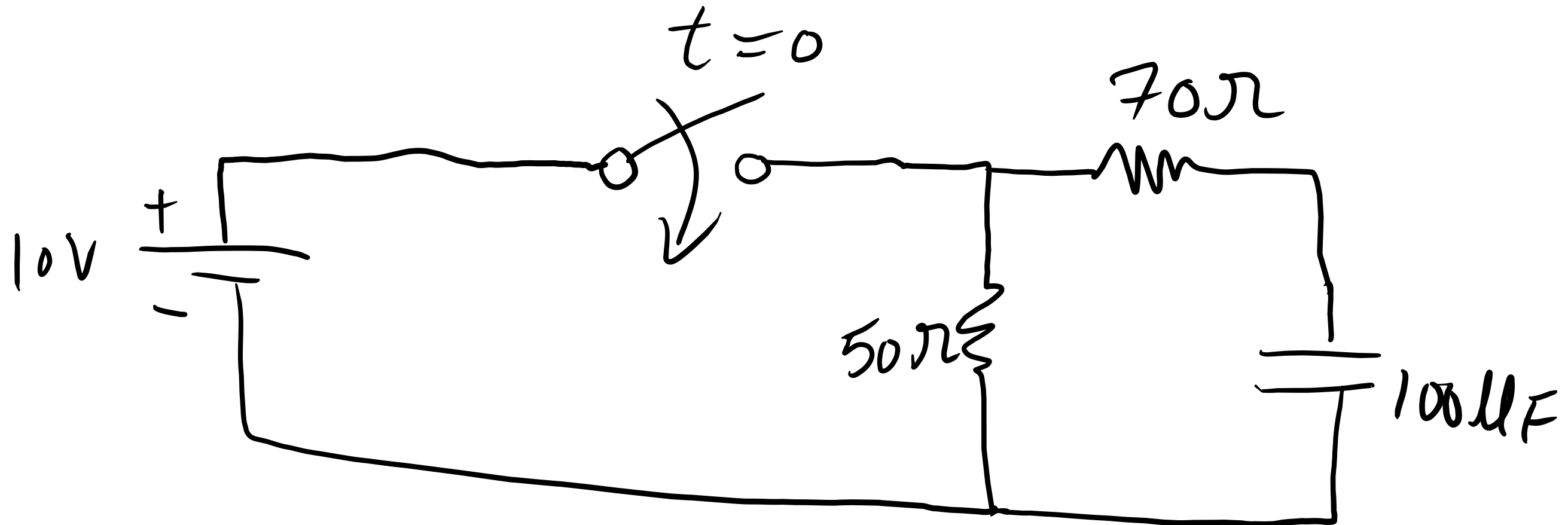In the circuit shown in figure below, if the switch is closed at time  $t = 0$ , find the time when the current from the battery reaches 250mA. Use classical method.



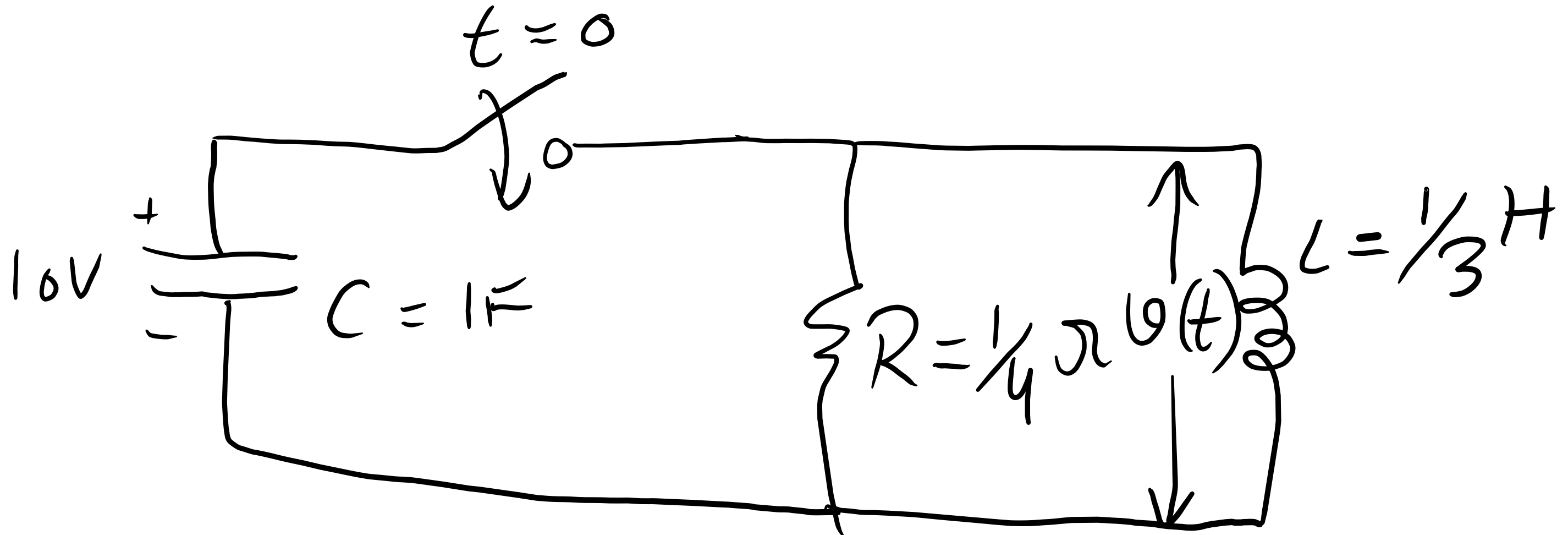In the circuit shown, capacitor C has an initial voltage  $V_C = 10$  volts and at the same instant, current through inductor L is zero. The switch is closed at time  $t = 0$ . Find out the expression for the voltage  $v(t)$  across the inductor L using classical method.



In the circuit shown in figure below, a switch  $S$  is in the position 1, for a long time and moved to position 2 at time  $t = 0$ . Find the voltage across capacitor for  $t > 0$ .

