

## UNIT VII

### FET AMPLIFIERS

#### 7.0 INTRODUCTION

Field Effect Transistor (FET) amplifiers provide an excellent voltage gain and high input impedance. Because of high input impedance and other characteristics of JFETs they are preferred over BJTs for certain types of applications.

There are 3 basic FET circuit configurations:

- i) Common Source
- ii) Common Drain
- iii) Common Gate

Similar to BJT CE, CC and CB circuits, only difference is in BJT large output collector current is controlled by small input base current whereas FET controls output current by means of small input voltage. In both the cases output current is controlled variable.

FET amplifier circuits use voltage controlled nature of the JFET. In Pinch off region,  $I_D$  depends only on  $V_{GS}$ .

#### 7.1 Common Source (CS) Amplifier

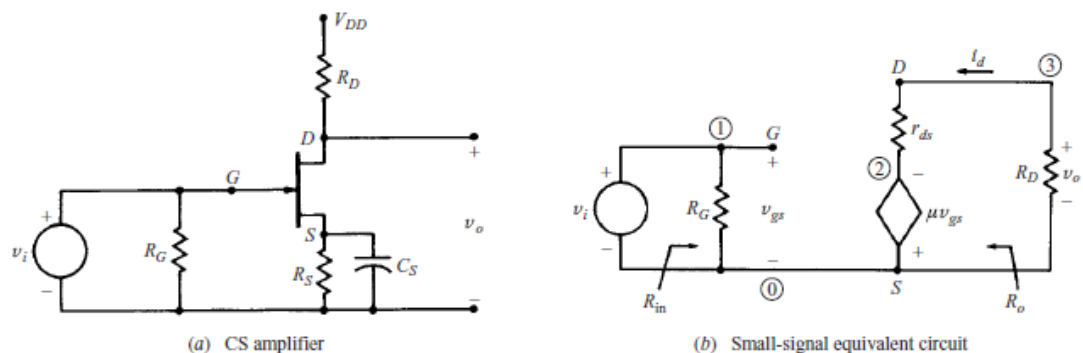


Fig. 7.1 (a) CS Amplifier (b) Small-signal equivalent circuit

A simple Common Source amplifier is shown in Fig. 7.1(a) and associated small signal equivalent circuit using voltage-source model of FET is shown in Fig. 7.1(b)

### Voltage Gain

Source resistance ( $R_S$ ) is used to set the Q-Point but is bypassed by  $C_S$  for mid-frequency operation. From the small signal equivalent circuit, the output voltage

$$V_O = -R_D \mu V_{gs} (R_D + r_d)$$

Where  $V_{gs} = V_i$ , the input voltage,

Hence, the voltage gain,

$$A_V = V_O / V_i = -R_D \mu (R_D + r_d)$$

### Input Impedance

From Fig. 7.1(b) Input Impedance is

$$Z_i = R_G$$

For voltage divider bias as in CE Amplifiers of BJT

$$R_G = R_1 \parallel R_2$$

### Output Impedance

Output impedance is the impedance measured at the output terminals with the input voltage

$$V_i = 0$$

From the Fig. 7.1(b) when the input voltage  $V_i = 0$ ,  $V_{gs} = 0$  and hence

$$\mu V_{gs} = 0$$

The equivalent circuit for calculating output impedance is given in Fig. 7.2.

$$\text{Output impedance } Z_o = r_d \parallel R_D$$

Normally  $r_d$  will be far greater than  $R_D$ . Hence  $Z_o \approx R_D$

## 7.2 Common Drain Amplifier

A simple common drain amplifier is shown in Fig. 7.2(a) and associated small signal equivalent circuit using the voltage source model of FET is shown in Fig. 7.2(b). Since voltage  $V_{gd}$  is more easily determined than  $V_{gs}$ , the voltage source in the output circuit is expressed in terms of  $V_{gs}$  and Thevenin's theorem.

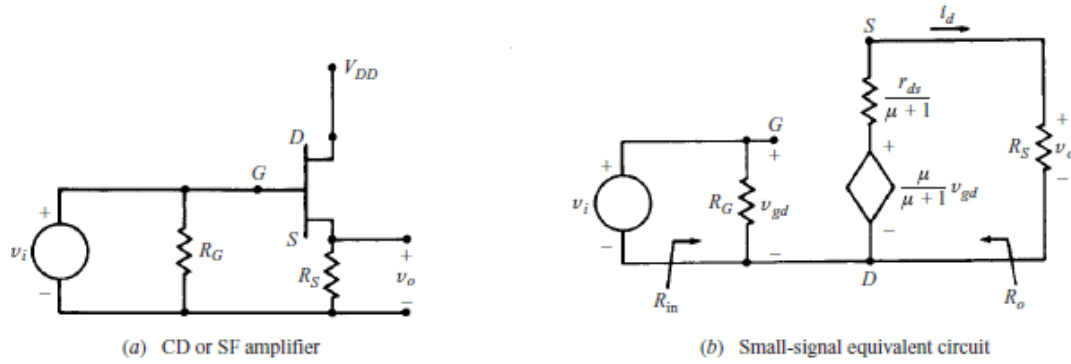


Fig. 7.2 (a)CD Amplifier (b)Small-signal equivalent circuit

### Voltage Gain

The output voltage,

$$V_O = R_S \mu V_{gd} / (\mu + 1) R_S + r_d$$

Where  $V_{gd} = V_i$  the input voltage.

Hence, the voltage gain,

$$A_v = V_O / V_i = R_S \mu / (\mu + 1) R_S + r_d$$

### Input Impedance

From Fig. 7.2(b), Input Impedance  $Z_i = R_G$

### Output Impedance

From Fig. 7.2(b), Output impedance measured at the output terminals with input voltage  $V_i = 0$  can be calculated from the following equivalent circuit.

As  $V_i = 0$ :  $V_{gd} = 0$ :  $\mu v_{gd} / (\mu + 1) = 0$

Output Impedance

$$Z_O = r_d / (\mu + 1) \parallel R_S$$

When  $\mu \gg 1$

$$Z_O = (r_d / \mu) \parallel R_S = (1/g_m) \parallel R_S$$

## 7.3 BIASING FET:-

For the proper functioning of a linear FET amplifier, it is necessary to maintain the operating point Q stable in the central portion of the pinch off region. The Q point should be independent of device parameter variations and ambient temperature variations.

This can be achieved by suitably selecting the gate to source voltage  $V_{GS}$  and drain current  $I_D$  which is referred to as biasing

JFET biasing circuits are very similar to BJT biasing circuits. The main difference between JFET circuits and BJT circuits is the operation of the active components themselves

There are mainly two types of Biasing circuits

1. Self bias
2. Voltage divider bias.

### 7.3.1. SELF BIAS:-

Self bias is a JFET biasing circuit that uses a source resistor to help reverse bias the JFET gate.

A self bias circuit is shown in the fig 7.3

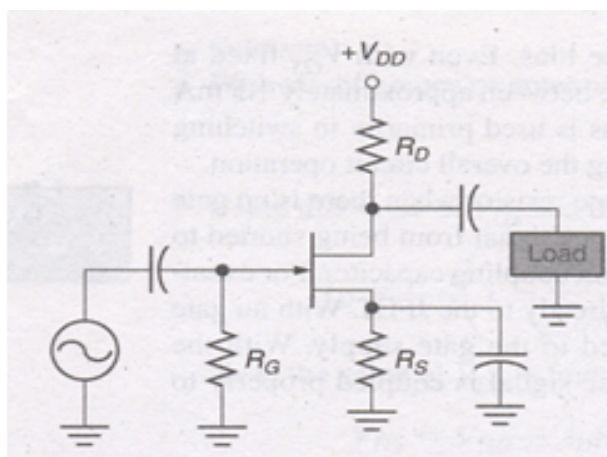


fig 7.3

Self bias is the most common type of JFET bias. This JFET must be operated such that gate source junction is always reverse biased. This condition requires a negative  $V_{GS}$  for an N channel JFET and a positive  $V_{GS}$  for P channel JFET. This can be achieved using the self bias arrangement as shown in Fig 7.3. The gate resistor  $R_G$  doesn't affect the bias because it has essentially no voltage drop across it, and the gate remains at 0V.  $R_G$  is necessary only to isolate an ac signal from ground in amplifier applications. The voltage drop across resistor  $R_S$  makes gate source junction reverse biased.

#### DC analysis of self Bias:-

In the following DC analysis, the N channel J FET shown in the fig7.4. is used for illustration.

For DC analysis we can replace coupling capacitors by open circuits and we can also replace the resistor  $R_G$  by a short circuit equivalent.

$$\therefore I_G = 0$$

The relation between  $I_D$  and  $V_{GS}$  is given by

$$I_d = I_{dss} \left[ 1 - \frac{V_{gs}}{V_p} \right]^2$$

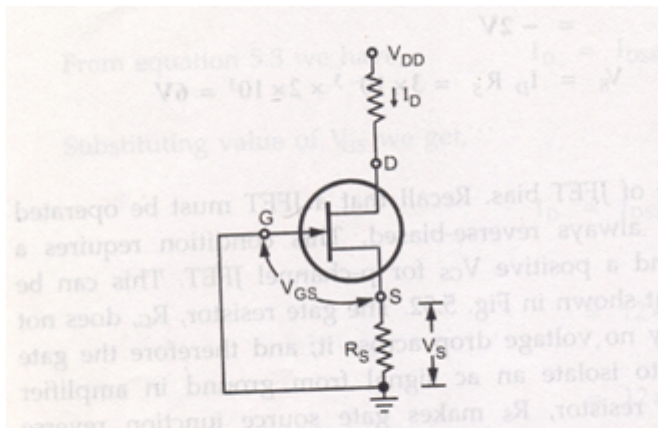


fig 7.4

$V_{GS}$  for N channel JFET is  $-I_D R_S$

Substituting this value in the above equation

$$I_d = I_{dss} \left[ 1 - \frac{(-I_d R_S)}{V_p} \right]^2$$

$$I_d = I_{dss} \left[ 1 + \frac{(I_d R_S)}{V_p} \right]^2$$

For the N-channel FET in the above figure

$I_S$  produces a voltage drop across  $R_S$  and makes the source positive w.r.t ground

In any JFET circuit all the source current passes through the device to drain circuit this is due to the fact that there is no significant gate current

therefore we can define source current as  $I_S = I_D$  and  $V_G = 0$  then

$$V_S = I_S R_S = I_D R_S$$

$$V_{GS} = V_G - V_S = 0 - I_D R_S = -I_D R_S$$

**Drawing the self bias line:-**

Typical transfer characteristics for a self biased JFET are shown in the fig 7.5.

The maximum drain current is 6mA and the gate source cut off voltage is -3V. This means the gate voltage has to be between 0 and -3V.

 


fig 7.5 Transfer characteristics

Now using the equation  $V_{GS} = -I_D R_s$  and assuming  $R_s$  of any suitable value we can draw the self bias line.

Let us assume  $R_s = 500\Omega$

With this  $R_s$ , we can plot two points corresponding to  $I_D = 0$  and  $I_D = I_{DSS}$

for  $I_D = 0$

$$V_{GS} = -I_D R_s$$

$$V_{GS} = 0 \times (500\Omega) = 0V$$

So the first point is (0 ,0)

$$(I_d, V_{GS})$$

For  $I_D = I_{DSS} = 6mA$


$$V_{GS} = (-6mA) (500\Omega) = -3V$$

So the 2<sup>nd</sup> Point will be (6mA,-3V)

By plotting these two points, we can draw the straight line through the points. This line will intersect the transconductance curve and it is known as self bias line. The intersection point gives the operating point of the self bias JFET for the circuit.

At Q point, the  $I_D$  is slightly  $>$  than 2mA and  $V_{GS}$  is slightly  $>$  -1V. The Q point for the self bias JFET depends on the value of  $R_s$ . If  $R_s$  is large, Q point far down on the transconductance curve,  $I_D$  is small, when  $R_s$  is small Q point is far up on the curve,  $I_D$  is large.

### 7.3.2 VOLTAGE DIVIDER BIAS:-

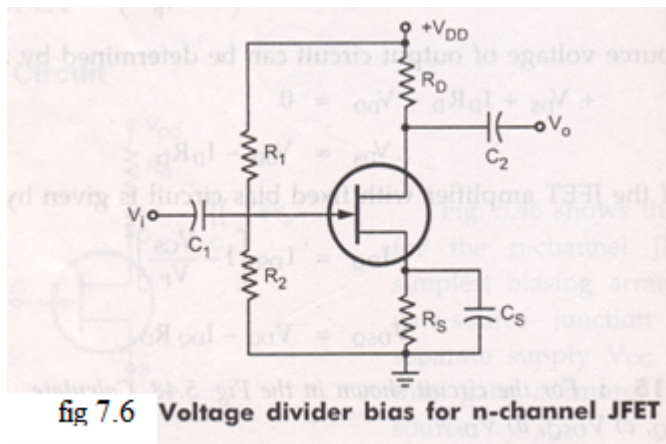


The fig7.6 shows N channel JFET with voltage divider bias. The voltage at the source of JFET must be more positive than the voltage at the gate in order to keep the gate to source junction reverse biased. The source voltage is

$$V_s = I_D R_s$$

The gate voltage is set by resistors R1 and R2 as expressed by the following equation using the voltage divider formula.

$$V_g = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$

For dc analysis fig 7.7

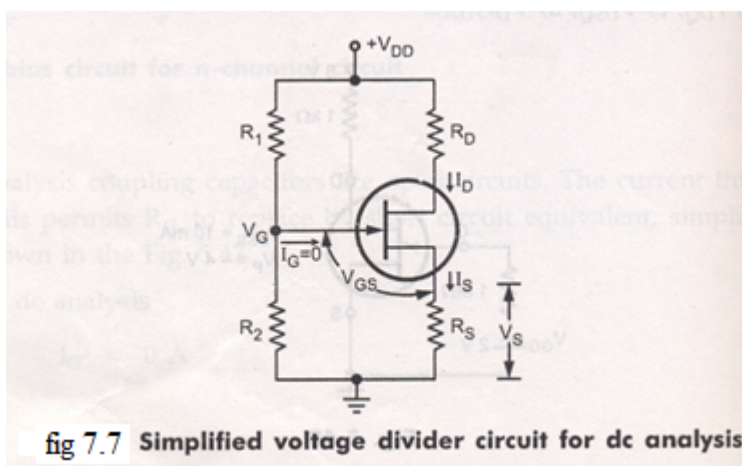

Applying KVL to the input circuit

$$V_G - V_{GS} - V_S = 0$$

$$\therefore V_{GS} = V_G - V_S = V_G - I_S R_S$$

$$V_{GS} = V_G - I_D R_S \quad \therefore I_S = I_D$$

Applying KVL to the input circuit we get

$$V_{DS} + I_D R_D + V_S - V_{DD} = 0$$

$$\therefore V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$


The Q point of a JFET amplifier, using the voltage divider bias is

$$I_{DQ} = I_{DSS} [1 - V_{GS}/V_P]^2$$

$$V_{DSQ} = V_{DD} - I_{DQ} (R_D + R_S)$$
 
## 7.4 JFET AS A VVR OR VDR:-

Let us consider the drain characteristics of FET as shown in the fig.



In this characteristics we can see that in the region before pinch off voltage, drain characteristics are linear, i.e. FET operation is linear. In this region the FET is useful as a voltage controlled resistor, i.e. the drain to source resistance is controlled by the bias voltage  $V_{GS}$ . (In this region only FET behaves like an ordinary resistor. This resistance can be varied by  $V_{GS}$ ). The operation of FET in this region is useful in most linear applications of FET. In such an application the FET is also referred to as a voltage variable resistor (VVR) or voltage dependent resistor (VDR).

The drain to source conductance ( $g_d$ )

$$g_d = \frac{I_D}{V_{DS}} \text{ for small values of } V_{DS} \text{ which may also be expressed as}$$

$$g_d = g_{d0} \left(1 - \frac{V_{GS}}{V_P}\right)^{1/2}$$



Where  $g_{d0}$  is the value of drain conductance


When the variation of the  $r_d$  with  $V_{GS}$  can be closely approximated by the expression

$$r_d = \frac{r_0}{1 - K V_{GS}} \quad \text{Where } r_0 = \text{drain resistance at zero gate bias. } K = \text{a constant, dependent upon}$$

FET type.
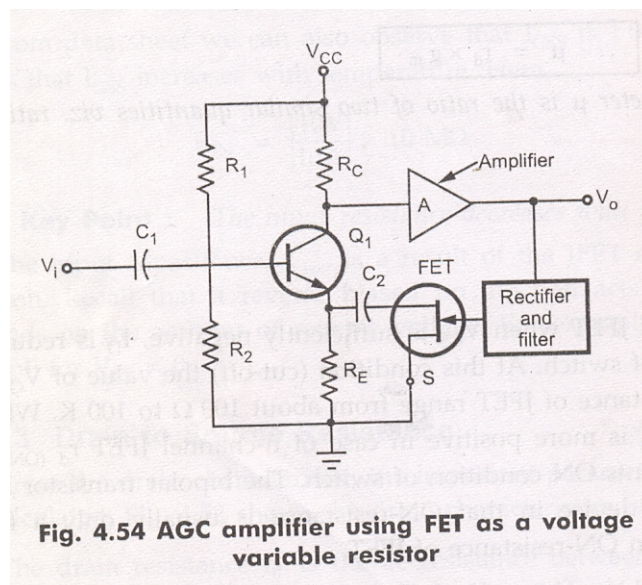
### 7.4.1 APPLICATION OF VVR

The VVR property of FET can be used to vary the voltage gain of a multistage amplifier A, as the signal level is increased. This action is called AGC automatic gain control. A typical arrangement is shown in the fig.




Here maximum value of signal is taken rectified; filter to produce a DC voltage proportional to the output signal level. This voltage is applied to the gate of JFET, this causing the resistance between drain and source to change. As this resistance is connected across  $R_E$ , so effective  $R_E$  also changes according to change in the drain to source resistance. When output signal level increases, the drain to source resistance  $r_d$  increases, increasing effective  $R_E$ . Increase in  $R_E$  causes the gain of transistor  $Q_1$  to decrease, reducing the output signal. Exactly reverse process takes place when output signal level decreased.

:: The output signal level is maintained constant. It is to be noted that the DC bias conditions of  $Q_1$  are not affected by JFET since FET is isolated from  $Q_1$  by capacitor  $C_2$
 
## 7.5 UNI JUNCTION TRANSISTOR (UJT)

Another device whose construction is similar to that of the FET is shown in the figure.




It is a three terminal device, having two layers. It consists of a slab of lightly doped N-type silicon material. The two base contacts are attached to both ends of this N-type surface. These are denoted as B1 and B2 respectively.

A P-type material is used to form a pn junction at the boundary of the aluminium rod and N-type slab. The N-type is lightly doped while P-type is heavily doped. That is N-type provides high resistivity and P-type provides low resistivity.

This device was originally described in the literature as the double-base diode, but is now commercially available under the designation Uni Junction transistor (UJT).

 
The standard symbol for this device is shown in the fig.



Here the emitter arrow is inclined and points toward B1 and This emitter arrow which is at an angle to the vertical line representing N-type material. This arrow indicates the direction of flow of conventional current when UJT is forward biased.

### EQUIVALENT CIRCUIT OF UJT

The circuit of UJT is shown in the fig.

 

In the construction ,the terminal emitter is closer to  $B_2$  as compared to  $B_1$ .

If we see the equivalent circuit of UJT, The internal resistances of the two bases are represented as  $R_{b1}$  and  $R_{b2}$ . Hence  $R_{b1}$  is greater than  $R_{b2}$ . The pn junction is represented by a normal diode with  $V_d$  as the drop across it. When the emitter diode is not conducting then the resistance between the two bases  $B_1$  and  $B_2$  is called interbase resistance denotes  $R_{bb}$

$$R_{bb}=R_{b1}+R_{b2}$$


Its value ranges from  $4k\Omega$  to  $12k\Omega$

### Intrinsic stand off ratio ( $\eta$ )


Consider UJT as shown in the fig. to which supply  $V_{bb}$  is connected. With  $I_e=0$ , That is emitter diode is not conducting ,

$$R_{bb}=R_{b1}+R_{b2}$$

 Then the voltage drop across  $R_{b1}$  can be obtained by using potential divider rule.



Replacing with its equivalent circuit

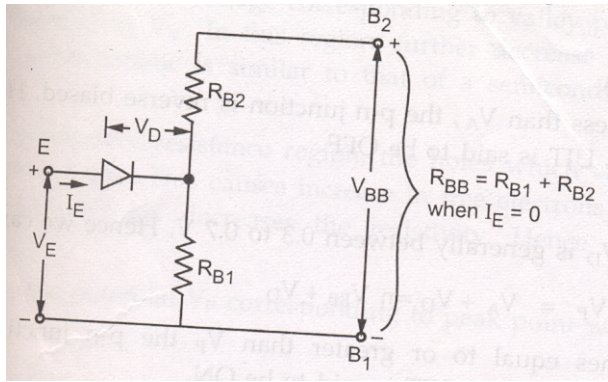

$$R_{bb} = R_{b1} + R_{b2}$$

When  $I_e = 0$


$$V_{RB1} = \left( \frac{R_{B1}}{R_{B1} + R_{B2}} \right) V_{BB} = \eta \cdot V_{BB} \text{ When } I_e = 0$$

$$\eta = \text{Intrinsic stand off ratio} = \left( \frac{R_{B1}}{R_{B1} + R_{B2}} \right) \text{ when } I_e = 0$$

$$\eta = \left( \frac{R_{B1}}{R_{BB}} \right) \text{ when } I_e = 0$$

The value of  $\eta$  is from 0.5 to 0.8 the voltage  $V_{rb1}$  is called intrinsic stand off voltage, because it keeps the emitter diode reverse biased for all emitter voltages less than  $V_{rb1}$ .

## Operation

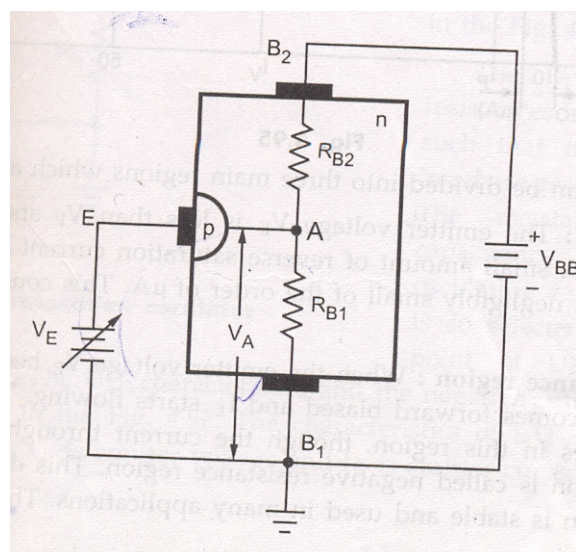

1. The supply  $V_{bb}$  is applied between  $B_2$  and  $B_1$ .

2. Variable emitter voltage  $V_e$  is applied across the emitter terminals.

3. If  $V_e$  is varied, potential of A is decided by  $\eta$  and is equal to  $\eta V_{bb}$

$$V_a = V_{rb1} = \eta V_{bb}$$

Case 1: If  $V_e < V_a$

As long as  $V_e < V_a$ , the pn junction is reverse biased. Hence emitter current  $I_e$  will not flow. Thus UJT is said to be off.

Case 2: if  $V_e > V_p$


The diode drop  $V_d$  is generally between 0.3 to 0.7v.

We can write  $V_p = V_a + V_d = \eta V_{bb} + V_d$

When  $V_e$  becomes equal to or greater than  $V_p$  the pn junction becomes forward biased and current  $I_e$  flows. Thus UJT is said to be ON.

## VI Characteristics

 1. The graph of  $I_e$  against emitter voltage plotted for a particular value of  $V_{bb}$  is called the characteristics of UJT.



The characteristics can be divided into three main regions.

1. cut off 2. Negative resistance region 3. Saturation region.

1. cut off: The  $V_e < V_p$  and the pn junction is reverse biased. A small amount of reverse saturation current  $I_{e0}$  flows through the device which is negligibly small of the order of micro amps. This condition remains till the peak point.

2. Negative resistance region: When emitter voltage  $V_e$  becomes equal to  $V_p$  then p n junction becomes forward biased and  $I_e$  starts flowing. The voltage across the device decreases in this region though the current through the device increases. Hence the region is called negative resistance region. This decreases the resistance  $R_{b1}$ . This region is stable and used in many applications. This region continues till valley point.

3. Saturation region: The region to the right of the valley point is called saturation region. In the valley point, the resistance changes from negative to positive. The resistance remains positive in the saturation region.

As  $V_{bb}$  increases , the potential  $V_p$  corresponding to peak point will increase.

### **Applications of UJT**

The UJT is mainly used in the triggering of other devices such as SCR. It is also used in the sawtooth wave generators and some timing circuits. The most popular application of UJT is as a relaxation oscillator to obtain short pulses for triggering of SCRs.

The relaxation oscillator using UJT which is ment for generating sawtooth waveform. It consists of a UJT and a capacitor , which is charged through emitter resistor as the supply voltage  $V_{bb}$  is switched ON.