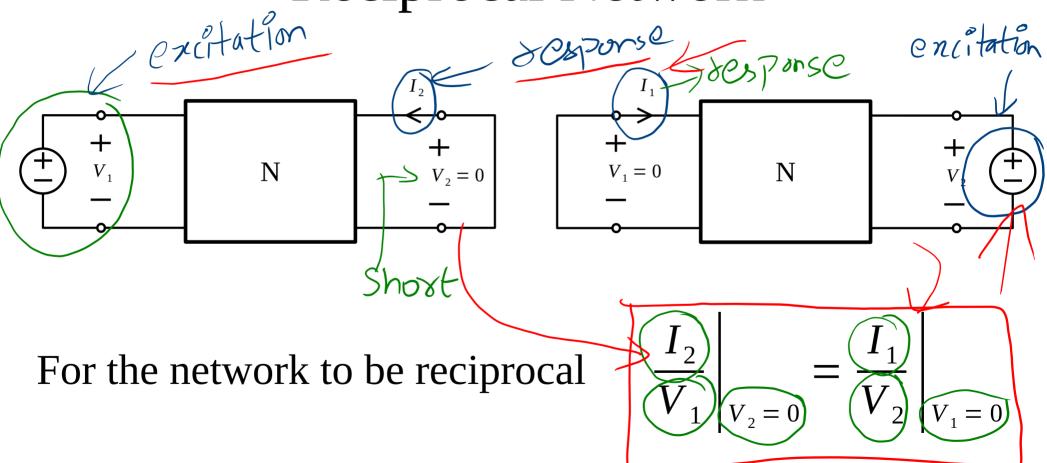


#### Reciprocal and Symmetrical Network


#### Reciprocal Network

- The *principle of reciprocity*, states that the <u>ratio of response</u> transform to the <u>excitation</u> transform remains identical even if the position of the response and excitation in the network are interchanged.
- Networks for which this condition holds are said to be *reciprocal*.
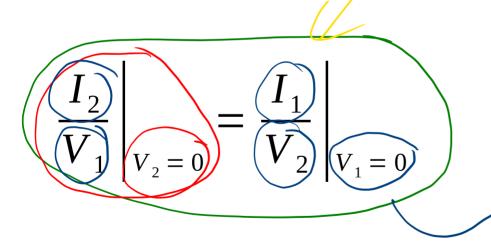
### Reciprocal Network



- Condition for reciprocal
   From the definition of z network
  - parameter:



$$V_1 = z_{11} I_1 + z_{12} I_2$$
  
 $V_2 = z_{21} I_1 + z_{22} I_2$ 

• Finding  $I_2/V_1$  for  $V_2=0$ , the expression of  $V_2$  now becomes:

$$V_{2} = \underbrace{z_{21}}_{21} I_{1} + \underbrace{z_{22}}_{12} I_{2}$$

$$0 = \underbrace{z_{21}}_{11} I_{1} + \underbrace{z_{22}}_{12} I_{2}$$

$$I_{1} = -\frac{z_{22}}{z_{21}} I_{2}$$

• Putting the value of  $I_1$  in the expression of  $V_1$ , we get:

$$V_{1} = z_{11} I_{1} + z_{12} I_{2} = z_{11} \left| \frac{z_{22}}{-z_{21}} I_{2} \right| + z_{12} I_{2}$$

Here,

$$V_{1} = \frac{-z_{11}}{z_{21}} = \frac{\Delta_{z}}{z_{21}} I_{2}$$

$$z_{11} z_{22} - z_{12} z_{21} = \Delta_{z}$$

$$V_{1} = -\frac{\Delta_{z}}{z_{21}} I_{2}$$

$$\therefore \frac{I_{2}}{V_{1}} = -\frac{Z_{21}}{\Delta_{z}} I_{2}$$

$$\therefore \frac{I_{2}}{V_{1}} = -\frac{Z_{21}}{\Delta_{z}} I_{2}$$

• Finding  $I_1/V_2$  for  $V_1=0$ , the expression of  $V_1$  now becomes:

$$\underbrace{V_{1} = z_{11} I_{1} + z_{12} I_{2}}_{0 = z_{11} I_{1} + z_{12} I_{2}} \qquad \qquad I_{2} = -\frac{z_{11}}{z_{12}} I_{1}$$

$$\underbrace{I_{2} = -\frac{z_{11}}{z_{12}} I_{1}}_{0 = z_{11} I_{1} + z_{12} I_{2}} \qquad \qquad I_{2} = -\frac{z_{11}}{z_{12}} I_{1}$$

• Putting the value of  $\underline{I_2}$  in the expression of  $\underline{V_2}$ , we get:


$$\underbrace{V_2 = z_{21} I_1 + z_{22} I_2}_{} = \underbrace{z_{21} I_1 + z_{22}}_{} \left| \frac{z_{11}}{-z_{12}} I_1 \right|^2$$

$$\begin{cases} V_2 = \underbrace{z_{12} z_{21} - z_{11} z_{22}}_{Z_{12}} I_2 = \underbrace{z_{12} z_{21}}_{Z_{12}} I_1 \end{cases}$$

Here, 
$$z_{11} z_{22} - z_{12} z_{21} = \Delta_{z_{12}}$$

$$\int V_2 = -\frac{\Delta_z}{Z_{12}} I_1$$
  $\therefore \left\{ \frac{I_1}{V_2} \right|_{V_1 = 0} = \left( -\frac{Z_{12}}{\Delta_z} \right)$ 

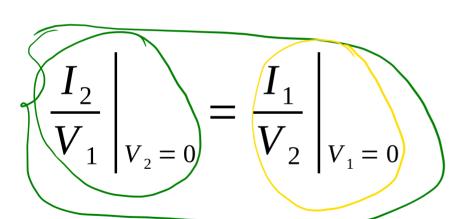• Condition for reciprocal • In terms of z parameter, network



we have:

$$\frac{Z_{21}}{\Delta_z} = -\frac{Z_{12}}{\Delta_z}$$


$$z_{21} = z_{12}$$


$$z_{12} = z_{21}$$

$$z_{12} = z_{21}$$


∴ For a <u>network to</u> be reciprocal

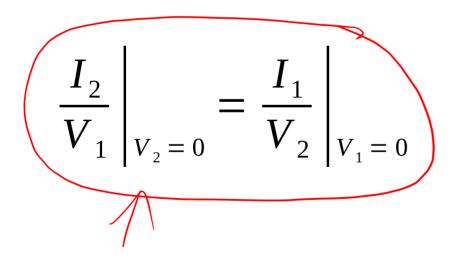- Condition for reciprocal
   From the definition of y network
  - parameter:



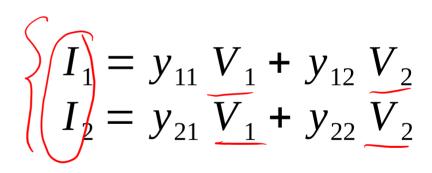

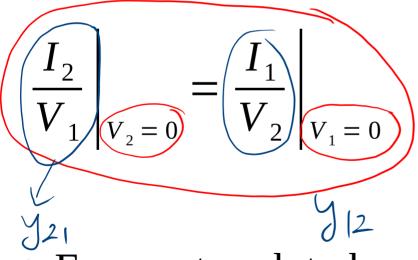- Condition for reciprocal
   In terms of y parameter, network
  - we have:




$$y_{21} = y_{12}$$

... For a network to be reciprocal

$$y_{12} = y_{21}$$
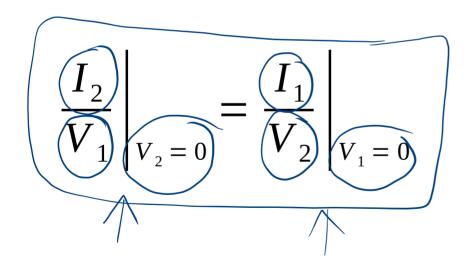
# Condition for **reciprocal** network (in terms of **transmission parameter**) (or, **T parameter**)

- Condition for reciprocal
   From the definition of T network
  - parameter:



$$\begin{cases} \widehat{V}_1 = A \ \underline{V}_2 - B \ \underline{I}_2 \\ \widehat{I}_1 = C \ \underline{V}_2 - D \ \underline{I}_2 \end{cases}$$

• Finding  $\underline{I_2/V_1}$  for  $\underline{V_2=0}$ , the expression of  $\underline{V_1}$  now becomes:

$$V_1 = A V_2 - B I_2$$

$$V_1 = -B I_2$$

$$\left| \frac{I_2}{V_1} \right|_{V_2 = 0} = -\frac{1}{B}$$

• Finding  $I_1/V_2$  for  $V_1=0$ , the expression of  $V_1$  now becomes:

$$\begin{array}{c}
V_{1} = A V_{2} - B I_{2} \\
0 = A V_{2} - B I_{2}
\end{array}$$

$$I_{2} = \frac{A}{B} V_{2}$$


• Putting the value of  $I_2$  in the expression of  $I_1$ , we get:

$$\left\langle \underbrace{I_1 = C \ V_2 - D \left(I_2\right)}_{2} = C \ V_2 - D \left(\frac{A}{B} \ V_2\right) \right\rangle$$


$$I_{1} = \frac{BC - AD}{B}V_{2} = -\frac{AD - BC}{B}V_{2}$$

$$\therefore \frac{I_{1}}{V_{2}}\Big|_{V_{1}=0} = -\frac{AD - BC}{B}$$

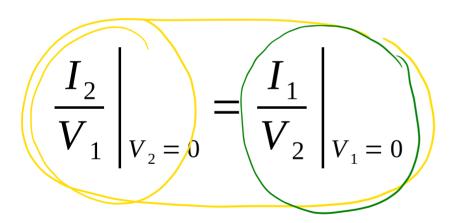• Condition for reciprocal • In terms of T parameter, network



we have:

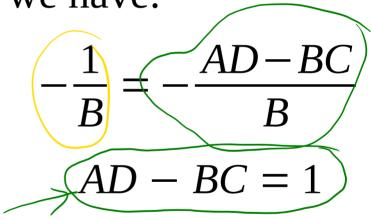


 $\therefore$  For a network to be reciprocal AD - BC = 1

# Condition for **reciprocal** network (in terms of **inverse transmission parameter** or, **T' parameter**)


• Condition for reciprocal network in terms of **T**' **parameters** is similar to the condition for reciprocal network in terms of **T parameters**.

So,

∴ For a network to be reciprocal

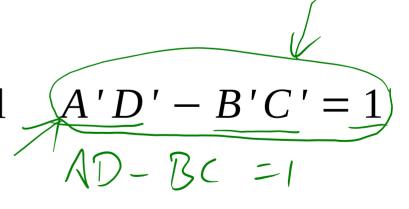

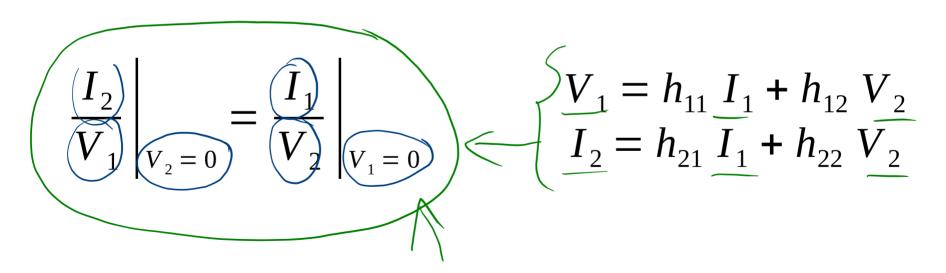- Condition for reciprocal
   From the definition of h network
  - parameter:



• Finding  $I_2/V_1$  for  $V_2=0$ , the expression of  $V_1$  now becomes:

$$\begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 \\ V_1 = h_{11} I_1 \end{cases} \qquad I_1 = \frac{1}{h_{11}} V_1$$

• Putting the value of  $I_1$  in the expression of  $I_2$ , we get:

$$\left\langle I_{2} = h_{21} \left( I_{1} \right) + h_{22} \left( V_{2} \right) = h_{21} \left| \frac{1}{h_{11}} V_{1} \right| = \frac{h_{21}}{h_{11}} V_{1}$$

$$I_{2} = \frac{h_{21}}{h_{11}} V_{1}$$

$$\therefore \underbrace{I_{2}}_{V_{1}} |_{V_{2} = 0} = \frac{h_{21}}{h_{11}}$$

• Finding  $(I_1/V_2)$  for  $V_1=0$ , the expression of  $V_1$  now becomes:


Decomes.  

$$V_1 = h_{11} I_1 + h_{12} V_2$$
 $I_1 = -\frac{h_{12}}{h_{11}} V_2$ 

$$\therefore V_2 = -\frac{h_{12}}{h_{11}} V_2$$

$$\therefore V_2 = -\frac{h_{12}}{h_{11}} V_2$$

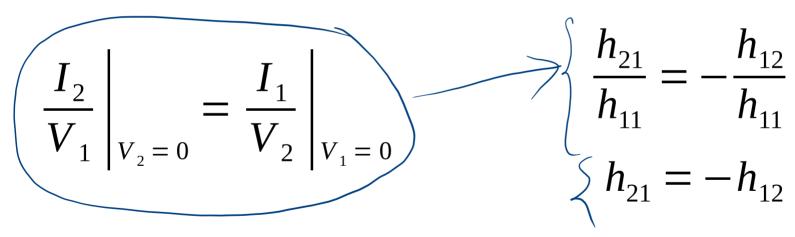- Condition for reciprocal In terms of h parameter, network
  - we have:



 $\therefore$  For a network to be reciprocal  $h_{12} = -h_{21}$ 

 Condition for reciprocal network in terms of g **parameters** is similar to the condition for reciprocal network in terms of **h parameters**.

 $\therefore$  For a network to be reciprocal  $(g_{12} = -g_{21})$ 

$$g_{12} = -g_{21}$$

## Condition for **reciprocal** network (in summary)


### Condition for **reciprocal** network


Parameter	Condition
$(\widehat{\mathbf{Z}})$	$Z_{12} = Z_{21}$
y	$y_{12} = y_{21}$
T	AD - BC = 1
T'	A'D' - B'C' = 1
h	$h_{12} = -h_{21}$
g	$g_{12} = -g_{21}$

### Symmetrical Network


• A two port network is termed as symmetrical if the input and output ports can be exchanged without altering the port voltages and currents.

### Symmetrical Network

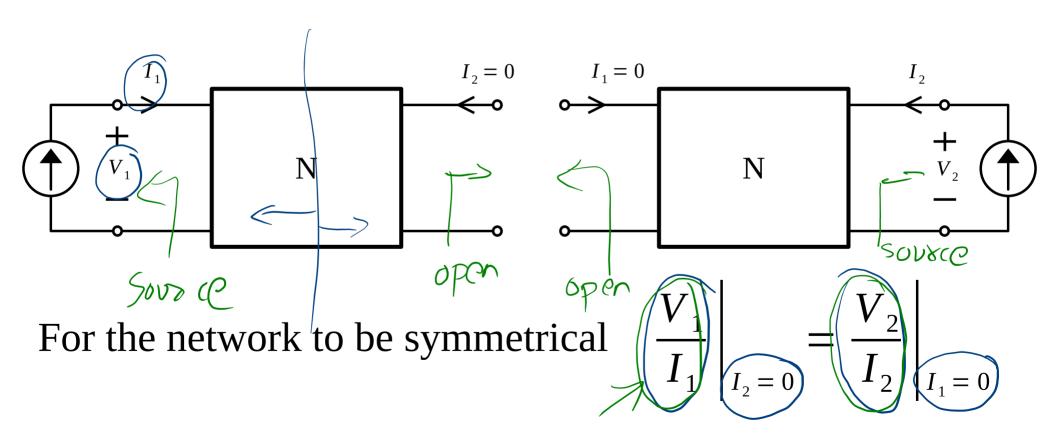

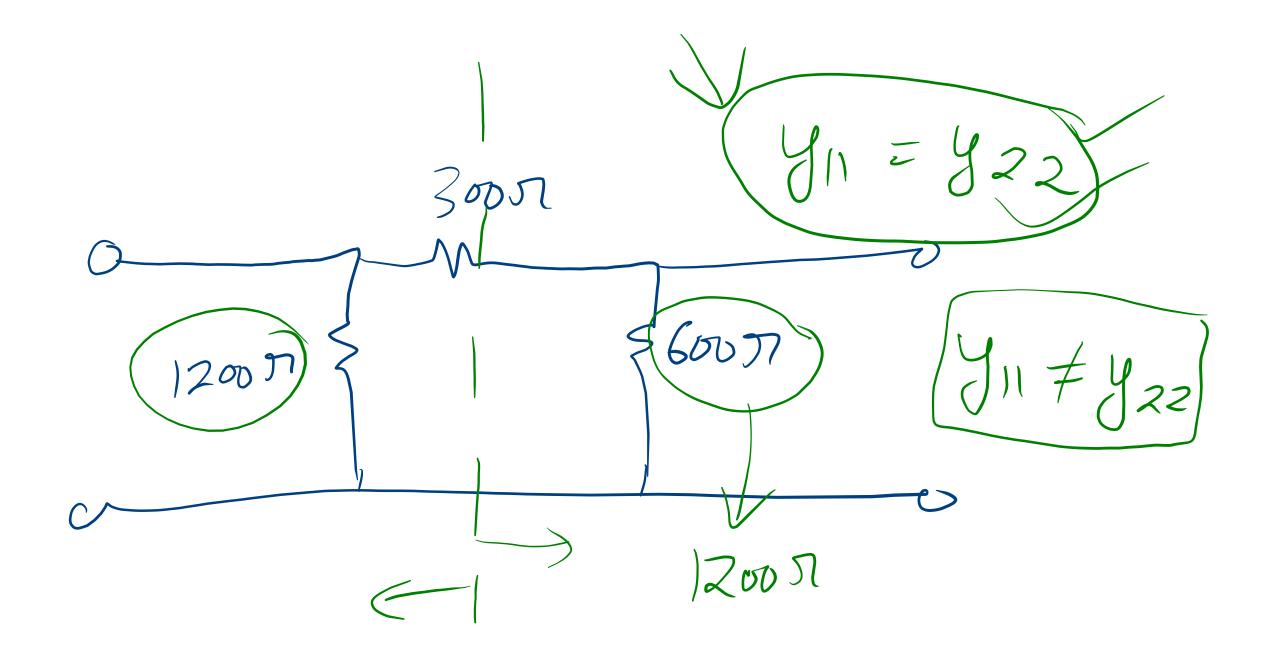


• Condition for symmetrical network

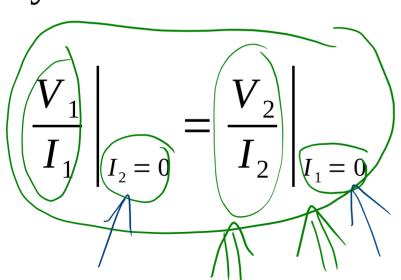

• From the definition of z parameter:

$$\begin{cases} V_1 = z_{11} I_1 + z_{12} I_2 \\ V_2 = z_{21} I_1 + z_{22} I_2 \end{cases}$$

• Condition for symmetrical network

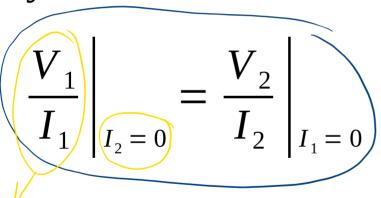


• In terms of z parameter, we have:

$$z_{11}=z_{22}$$

 $\stackrel{\smile}{:}$  For a network to be symmetrical  $z_{11} = z_{22}$ 

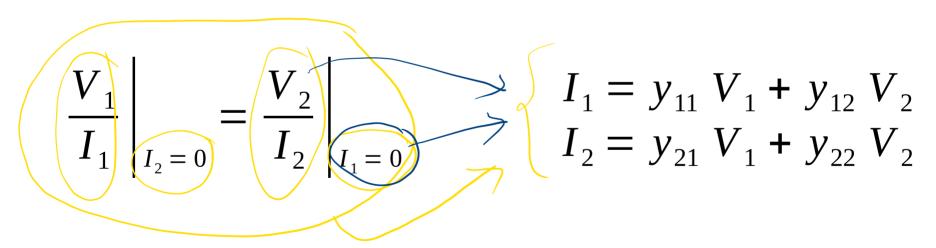 Condition for symmetrical network • From the definition of y parameter:



• Finding  $V_1/I_1$  for  $I_2$ =0, the expression of  $I_2$  now becomes:

$$\begin{aligned}
SI_2 &= y_{21} V_1 + y_{22} V_2 \\
0 &= y_{21} V_1 + y_{22} V_2
\end{aligned}
\qquad V_2 = -\frac{y_{21}}{y_{22}} V_1$$

• Putting the value of V<sub>2</sub> in the expression of I<sub>1</sub>, we get:

$$\underbrace{I_1 = y_{11} V_1 + y_{12} V_2}_{I_1} = y_{11} V_1 + y_{12} - \frac{y_{21}}{y_{22}} V_1$$

$$\begin{cases} I_{1} = y_{11} V_{1} + y_{12} \middle| -\frac{y_{21}}{y_{22}} V_{1} \middle| = \underbrace{\frac{y_{11} y_{22} - y_{12} y_{21}}{y_{22}}}_{y_{22}} V_{1} \end{cases}$$
Here,
$$\begin{cases} Y_{11} y_{22} - y_{12} y_{21} = \Delta_{y} \\ So, \end{cases}$$

$$\begin{cases} I_{1} = \frac{\Delta_{y}}{y_{22}} V_{1} \\ \vdots \\ I_{1} \middle|_{I_{2} = 0} \end{cases} = \underbrace{\frac{y_{22}}{\Delta_{y}}}_{I_{2}} \end{cases}$$

• Finding  $V_2/I_2$  for  $I_1$ =0, the expression of  $I_1$  now becomes:

$$\begin{cases} I_{1} = y_{11} V_{1} + y_{12} V_{2} \\ 0 = y_{11} V_{1} + y_{12} V_{2} \end{cases} = -\frac{y_{12}}{y_{11}} V_{2}$$

• Putting the value of  $V_1$  in the expression of  $I_2$ , we get:

get:  

$$I_2 = y_{21}V_1 + y_{22}V_2 = y_{21} - \frac{y_{12}}{y_{11}}V_2 + y_{22}V_2$$


$$\begin{cases} I_2 = y_{21} \left| -\frac{y_{12}}{y_{11}} V_2 \right| + y_{22} V_2 = \underbrace{y_{11} y_{22} - y_{12} y_{21}}_{y_{11}} V_2 \end{cases}$$

Here,

$$y_{11} \ y_{22} - y_{12} \ y_{21} = \Delta_y$$

So, 
$$C I_{2} = \frac{\Delta_{y}}{y_{11}} V_{2}$$
  $\therefore \frac{V_{2}}{I_{2}} \Big|_{I_{1}=0} = \frac{y_{11}}{\Delta_{y}}$ 

 Condition for symmetrical network

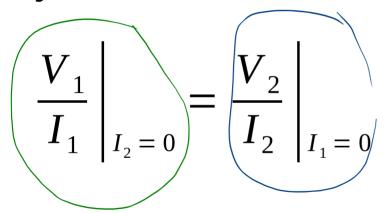


• In terms of y parameter, we have:

$$\frac{y_{22}}{\Delta_y} = \frac{y_{11}}{\Delta_y}$$

$$y_{22} = y_{11}$$

$$\frac{y_{22}}{\Delta_y} = y_{11}$$


∴ For a network to be symmetrical

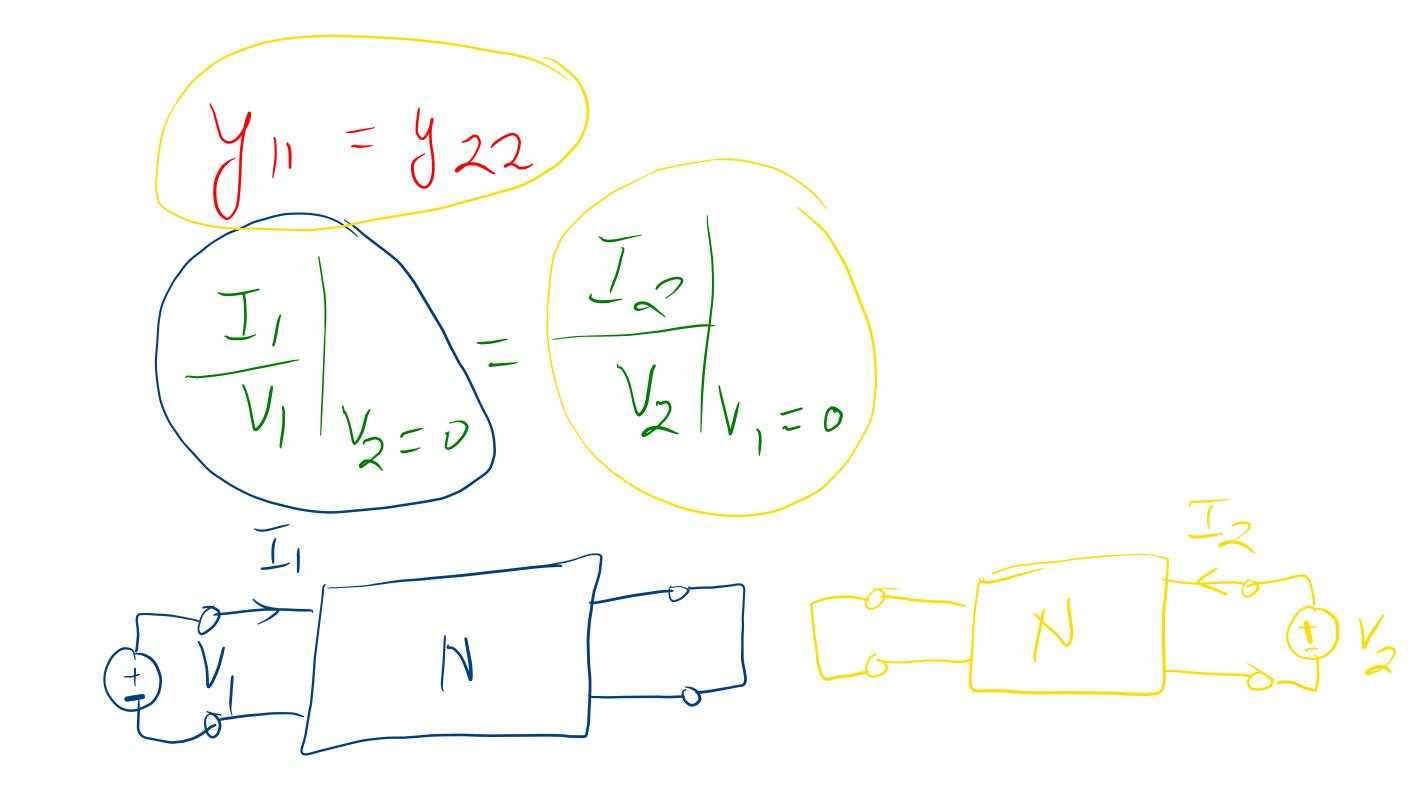

# Condition for **symmetrical** network (in terms of **transmission parameter**) (or, **T parameter**)

• Condition for symmetrical network

• From the definition of T parameter:

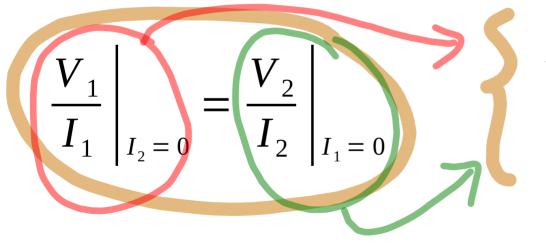

$$V_1 = A V_2 - B I_2$$
  
 $I_1 = C V_2 - D I_2$ 

• Finding V<sub>1</sub>/I<sub>1</sub> for I<sub>2</sub>=0, the expression of V<sub>1</sub> now becomes:

$$V_{1} = A V_{2} - B I_{2}$$

$$V_{1} = A V_{2}$$

$$V_{2} = \frac{1}{A} V_{1}$$

• Putting the value of V<sub>2</sub> in the expression of I<sub>1</sub>, we get:

$$I_1 = C(V_2 - D I_2) = C \left| \frac{1}{A} V_1 \right| = \frac{C}{A} V_1$$

$$I_1 = \frac{C}{A} V_1$$


$$\therefore \left| \frac{V_1}{I_1} \right|_{I_2 = 0} = \frac{A}{C}$$

• Finding  $V_2/I_2$  for  $I_1$ =0, the expression of  $I_1$  now becomes:

$$I_1 = C V_2 - D I_2$$
 $C V_2 = D I_2$ 
 $C V_2 = D I_2$ 

$$\therefore \left| \frac{V_2}{I_2} \right|_{I_1 = 0} = \left| \frac{D}{C} \right|$$

• Condition for symmetrical network

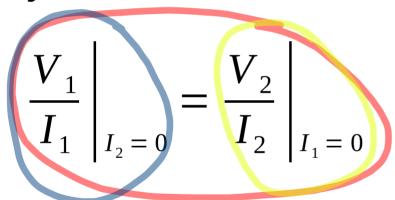

• In terms of T parameter, we have:

$$\frac{A}{C} = \frac{D}{C}$$

$$A = D$$

 $\therefore$  For a network to be symmetrical A = D

# Condition for symmetrical network (in terms of inverse transmission parameter or, T' parameter)


 Condition for symmetrical network in terms of T' **parameters** is similar to the condition for symmetrical network in terms of **T parameters**.

So,

 $\therefore$  For a network to be symmetrical A' = D'

$$A' = D$$

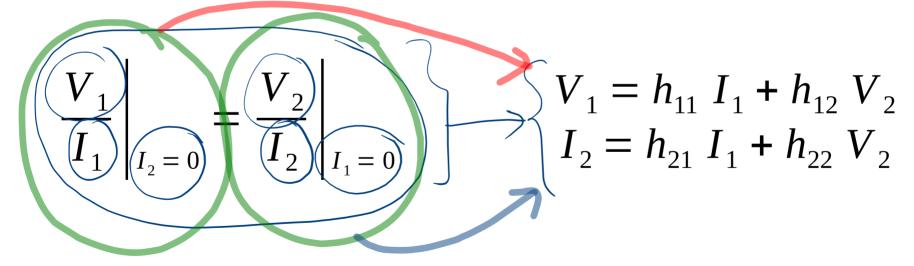 Condition for symmetrical network • From the definition of h parameter:



• Finding V<sub>1</sub>/I<sub>1</sub> for I<sub>2</sub>=0, the expression of I<sub>2</sub> now becomes:

$$I_{2} = h_{21} I_{1} + h_{22} V_{2}$$

$$0 = h_{21} I_{1} + h_{22} V_{2}$$

$$V_{2} = -\frac{h_{21}}{h_{22}} I_{1}$$

• Putting the value of V<sub>2</sub> in the expression of V<sub>1</sub>, we get:


$$V_1 = h_{11} I_1 + h_{12} V_2 = h_{11} I_1 + h_{12} - \frac{h_{21}}{h_{22}} I_1$$

• Finding  $V_2/I_2$  for  $I_1=0$ , the expression of  $I_2$  now becomes:

$$\begin{array}{c|c}
I_2 = h_{21} I_1 + h_{22} V_2 \\
I_2 = h_{22} V_2
\end{array}
\qquad \therefore \begin{array}{c|c}
V_2 \\
I_1 = 0
\end{array}
= \frac{1}{h_{22}}$$

• Condition for symmetrical network



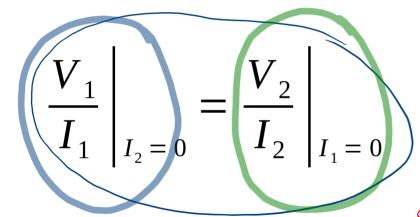

$$\frac{\Delta_h}{h_{22}} = -\frac{1}{h_{22}}$$

$$\Delta_h = 1$$

 $\therefore$  For a network to be reciprocal  $\Delta_h = 1$ 

• Condition for symmetrical network in terms of **g parameters** is similar to the condition for symmetrical network in terms of **h parameters**.

 $\therefore$  For a network to be reciprocal  $(\Delta_g = 1)$ 

Here, 
$$g_{11}$$
  $g_{22}$  –  $g_{12}$   $g_{21}$  =  $\Delta_g$ 

#### Condition for **symmetrical** network (in summary)

#### Condition for **symmetrical** network

Parameter	Condition
Z	$z_{11} = z_{22}$
y	$y_{11} = y_{22}$
ABCD	A = D
A'B'C'D'	A' = D'
h 3	$\Delta_h = 1$
g	$\Delta_g = 1$

a , tx(a) 

#### Relationship and transformation between sets of parameters

#### Relationship and transformation between sets of parameters

- Once we know a set of parameters of a network, than based on our needs, we can find the remaining five sets of parameter in terms of the known parameter.
- It is a simple matter to find the relationships of the sets of parameters.

#### z-parameter in terms of y-parameter

 From the definition of y
 From the definition of z parameter:

$$\begin{cases} I_{1} = y_{11} V_{1} + y_{12} V_{2} \\ I_{2} = y_{21} V_{1} + y_{22} V_{2} \end{cases} \qquad \begin{cases} V_{1} = \underline{z}_{11} I_{1} + z_{12} I_{2} \\ V_{2} = z_{21} I_{1} + z_{22} I_{2} \end{cases}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

parameter:

$$\begin{cases} V_{1} = \underline{z_{11}} \ I_{1} + z_{12} \ I_{2} \\ V_{2} = \underline{z_{21}} \ I_{1} + z_{22} \ I_{2} \end{cases}$$

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

#### z-parameter in terms of y-parameter

• From the definition of y parameter:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

• From the definition of z parameter:

$$\begin{bmatrix} \boldsymbol{V}_1 \\ \boldsymbol{V}_2 \end{bmatrix} = \begin{bmatrix} \boldsymbol{z}_{11} & \boldsymbol{z}_{12} \\ \boldsymbol{z}_{21} & \boldsymbol{z}_{22} \end{bmatrix} \begin{bmatrix} \boldsymbol{I}_1 \\ \boldsymbol{I}_2 \end{bmatrix}$$

$$[I] = [y][V]$$

$$[V] = [y]^{-1}[I]$$

$$|V| = |z| |I|$$

$$\therefore [z] = [y]^{-1}$$

#### **z-parameter** in terms of **y-parameter**

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y \end{bmatrix}^{-1}$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \frac{1}{\Delta_y} \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}$$

$$z_{11} = \frac{y_{22}}{\Delta_y} \quad z_{12} = -\frac{y_{12}}{\Delta_y} \quad z_{21} = -\frac{y_{21}}{\Delta_y} \quad z_{22} = \frac{y_{11}}{\Delta_y}$$

[ y7 - ] = - [ J22 - J21 ]

Ay [ -y12 - y11 ] - 1 | y22 - y12 | - y21 | y11 | 121 | y22 | - y12 | y11 | |

#### z-parameter in terms of T-parameter

- From the definition of T parameter:
- From the definition of z parameter:

$$\begin{cases} V_1 = A V_2 - B I_2 \\ I_1 = C V_2 - D I_2 \end{cases}$$

• Rewriting the expression of I<sub>1</sub> from the definition of T-parameter, we get:

$$I_1 = C V_2 - D I_2 \Rightarrow V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2$$

#### z-parameter in terms of T-parameter

$$V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2$$

• Putting the value of V<sub>2</sub> in the expression of V<sub>1</sub>, we get:

$$V_1 = A(V_2) - B I_2 = A \left| \frac{1}{C} I_1 + \frac{D}{C} I_2 \right| - B I_2$$

$$\widehat{V}_{1} = \frac{A}{C} \widehat{I}_{1} + \frac{A}{C} \widehat{I}_{2} - B I_{2} = \underbrace{A}_{C} \widehat{I}_{1} + \underbrace{AD - BC}_{C} \widehat{I}_{2}$$

$$V_1 = \frac{A}{C} I_1 + \frac{A D - B C}{C} I_2 = \frac{A}{C} I_1 + \frac{\Delta_T}{C} I_2$$

Here,

$$AD - BC = \Delta_T$$

• From T parameter, we have

$$(V_1) = \frac{A}{C}(I_1) + \frac{\Delta_T}{C}(I_2) \text{ and } (V_2) = \frac{1}{C}(I_1) + \frac{D}{C}(I_2)$$

• From the definition of T parameter:

$$\begin{cases} V_1 = \frac{A}{C} I_1 + \frac{\Delta_T}{C} I_2 \\ V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2 \end{cases}$$

• From the definition of z parameter:

$$z_{11} = \frac{A}{C} \qquad z_{12} = \underbrace{\Delta_T}_{C} \qquad z_{21} = \underbrace{C}_{C} \qquad z_{22} = \underbrace{D}_{C}$$

- From the definition of h parameter:
- From the definition of z parameter:

$$\begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 \\ I_2 = h_{21} I_1 + h_{22} V_2 \end{cases} \longrightarrow \begin{cases} V_1 = z_{11} I_1 + z_{12} I_2 \\ V_2 = z_{21} I_1 + z_{22} I_2 \end{cases}$$

• Rewriting the expression of I<sub>2</sub> from the definition of h-parameter, we get:

$$I_{2} = h_{21} I_{1} + h_{22} V_{2} \Rightarrow V_{2} = -\frac{h_{21}}{h_{22}} I_{1} + \frac{1}{h_{22}} I_{2}$$

$$V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2$$

• Putting the value of  $V_2$  in the expression of  $V_1$ , we get:

$$\underbrace{V_{1}} = \underbrace{h_{11} I_{1} + h_{12} \underbrace{V_{2}}_{1} = h_{11} I_{1} + h_{12}}_{11} + \underbrace{\frac{h_{21}}{h_{22}} I_{1} + \frac{1}{h_{22}} I_{2}}_{12} + \underbrace{\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} I_{1}}_{1} + \underbrace{\frac{h_{12}}{h_{22}} I_{2}}_{12} + \underbrace{\frac{h_{12}}{h_{22}} I_{2}}_{12}$$

$$V_{1} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} I_{1} + \frac{h_{12}}{h_{22}} I_{2} = \underbrace{\frac{\Delta_{h}}{h_{22}} I_{1} + \frac{h_{12}}{h_{22}} I_{2}}_{\text{Here.}}$$

$$(h_{11} h_{22} - h_{12} h_{21} = \Delta_h)$$

• From h parameter, we have

$$V_1 = \frac{\Delta_h}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2$$
 and  $V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2$ 

• From the definition of h parameter:

• From the definition of z parameter:

$$\underbrace{V_{1}}_{1} = z_{11} \underbrace{I_{1}}_{1} + z_{12} \underbrace{I_{2}}_{2} 
\underbrace{V_{2}}_{1} = z_{21} \underbrace{I_{1}}_{1} + z_{22} \underbrace{I_{2}}_{2}$$

$$z_{11} = \frac{\Delta_h}{h_{22}}$$

$$z_{12} = \frac{h_{12}}{h_{22}}$$

$$z_{21} = -\frac{h_{21}}{h_{22}}$$

$$z_{22} = \frac{1}{h_{22}}$$

$$y_{12}$$
  $-\frac{Z_{12}}{\Delta_z}$   $-\frac{\Delta_T}{B}$   $y_{21}$   $-\frac{Z_{21}}{\Delta_z}$   $-\frac{1}{B}$   $y_{22}$   $\frac{Z_{11}}{\Delta_z}$   $\frac{A}{B}$  Here,  $\Delta_x = x_{11} \ x_{22} - x_{12} \ x_{21}$ 

 $y_{11}$ 

 $h_{12}$  $g_{12}$  $g_{22}$  $h_{21}$  $g_{21}$  $g_{22}$  $g_{22}$ 

$$h \quad \frac{z}{\Delta_{z}} \quad \frac{y}{1} \quad \frac{T}{B} \quad \frac{T'}{A'} \quad \frac{g}{\Delta_{g}}$$

$$h_{11} \quad \frac{\lambda_{z}}{z_{22}} \quad \frac{1}{y_{11}} \quad \frac{B}{D} \quad \frac{B'}{A'} \quad \frac{g_{22}}{\Delta_{g}}$$

$$h_{12} \quad \frac{z_{12}}{z_{22}} \quad -\frac{y_{12}}{y_{11}} \quad \frac{\Delta_{T}}{D} \quad \frac{1}{A'} \quad -\frac{g_{12}}{\Delta_{g}}$$

$$h_{21} \quad -\frac{z_{21}}{z_{22}} \quad \frac{y_{21}}{y_{11}} \quad -\frac{1}{D} \quad -\frac{\Delta_{T'}}{A'} \quad -\frac{g_{21}}{\Delta_{g}}$$

$$\sqrt{h_{22}} \quad \frac{1}{z_{22}} \quad \frac{\Delta_{y}}{y_{11}} \quad \frac{C}{D} \quad \frac{C'}{A'} \quad \frac{g_{11}}{\Delta_{g}}$$

$$g_{11} = \frac{z}{1} - \frac{y}{y_{22}} = \frac{T}{A} - \frac{T'}{D'} = \frac{h}{h_{22}}$$

$$g_{11} = \frac{1}{z_{11}} - \frac{\lambda_y}{y_{22}} - \frac{\Delta_T}{A} - \frac{1}{D'} - \frac{h_{12}}{\Delta_h}$$

$$g_{12} = \frac{z_{12}}{z_{11}} - \frac{y_{12}}{y_{22}} - \frac{1}{A} - \frac{1}{D'} - \frac{h_{12}}{\Delta_h}$$

$$g_{21} = \frac{z_{21}}{z_{11}} - \frac{y_{21}}{y_{22}} - \frac{1}{A} - \frac{\Delta_{T'}}{D'} - \frac{h_{21}}{\Delta_h}$$

$$g_{22} = \frac{\Delta_z}{z_{11}} - \frac{1}{y_{22}} - \frac{B}{A} - \frac{B'}{D'} - \frac{h_{11}}{\Delta_h}$$
Here,  $\Delta_x = x_{11} x_{22} - x_{12} x_{21}$ 

d'ilde )2 multiply